



Computer Systems and Networks

ECPE 170 – Jeff Shafer – University of the Pacific

State Machines & Karnaugh Maps

Upcoming Events

➤ **Homework 5 - Due Tuesday**

- Paper submissions accepted for this assignment (since it involves drawing Karnaugh Maps...)

Upcoming Events

➤ Quiz 2 - Tuesday

➤ Topics *may or may not* include:

- Simplifying Boolean expressions with identities?
- Sum-of-products or product-of-sum form?
- Converting between a truth table and a circuit diagram (with logic gates)?
- Common combinational circuits: decoders, multiplexers?
 - Basic operation of these devices, i.e. inputs and outputs
- Sequential circuits: SR, JK, D flip-flops?
 - Basic operation of these devices, i.e. inputs and outputs

Recap from Last Class




- **Why do real hardware devices use NAND / NOR gates instead of AND / OR / NOT gates?**
 - These are “universal” gates – any function can be made using only NAND or only NOR gates
 - Simplifies manufacturing to use the same gate type
- **What is the difference between combinational and sequential circuits?**
 - **Combinational** – output is based on input only
 - **Sequential** – output is based on input and current output (or “state”)

Recap from Last Class

- **What is the difference between a half-adder and a full-adder?**
 - **Half adder** adds two inputs (x , y) and produces sum and carry-out
 - **Full adder** adds three inputs (x , y , carry-in) and produces sum and carry-out
 - We build it out of two half-adders!

Recap from Last Class

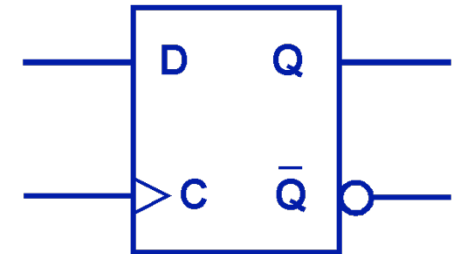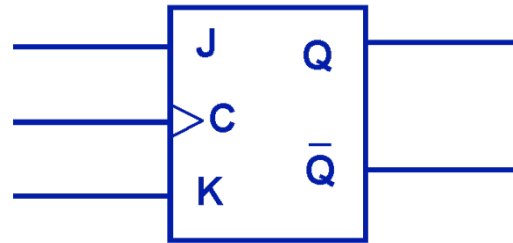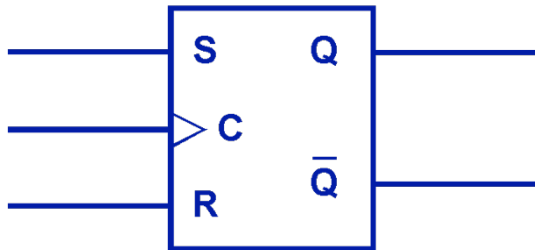➔ What are the outputs of these common flip-flops?



S	R	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	undefined

J	K	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$

D	$Q(t+1)$
0	0
1	1

Discussion

- Engineering lab equipment and facilities
 - Partially paid for from your lab fee \$\$
 - Suggestions for improvement?

State Machines




State Machines


- How do we design complicated sequential systems?
 - **Finite State Machine (FSM)**
 - In visual form
 - A set of nodes that hold the states of the machine
 - A set of arcs that connect the states
- Two different types of state machines: **Moore** and **Mealy**
 - Both produce systems that produce the same output
 - Differ only in how the output of the machines are expressed
- Moore: place outputs on each node
- Mealy: present outputs on the transitions

JK Flip-Flop in State Machine Form

Moore FSM

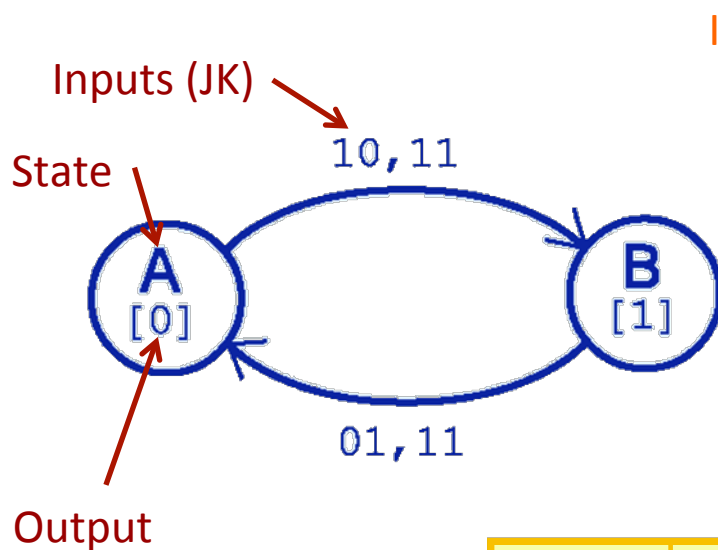

Mealy FSM


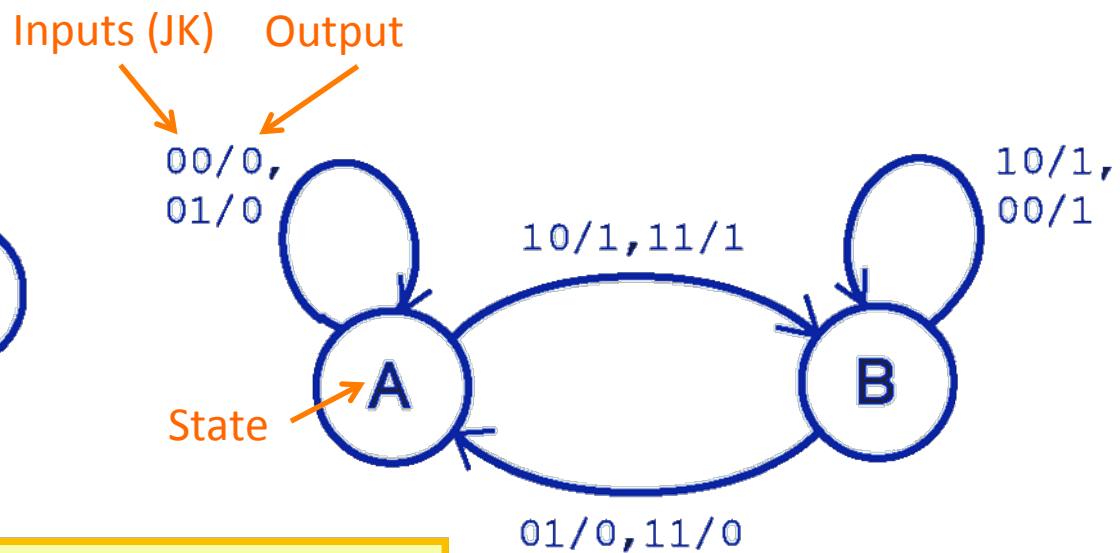


J	K	Q(t+1)
0	0	Q(t) (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$

Different Implementations

- Although the behavior of Moore and Mealy machines is identical, their implementations differ:


Moore machine:

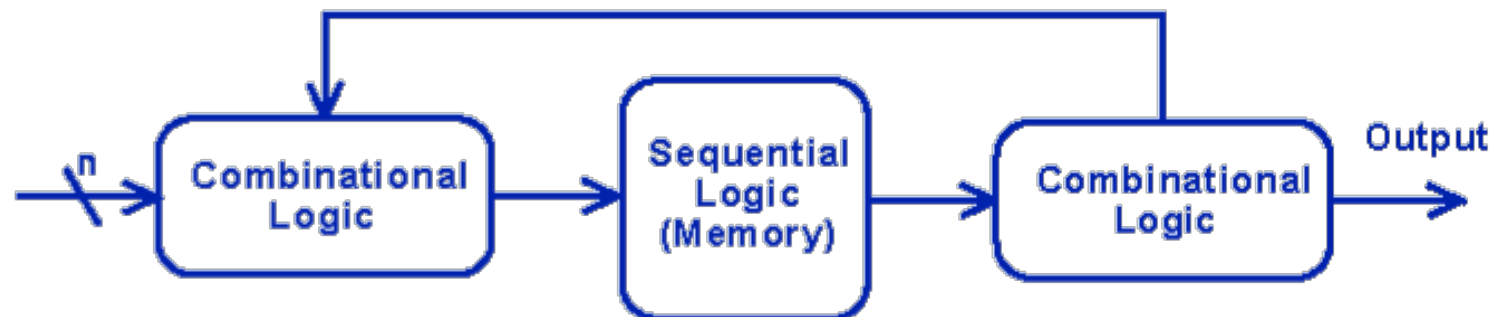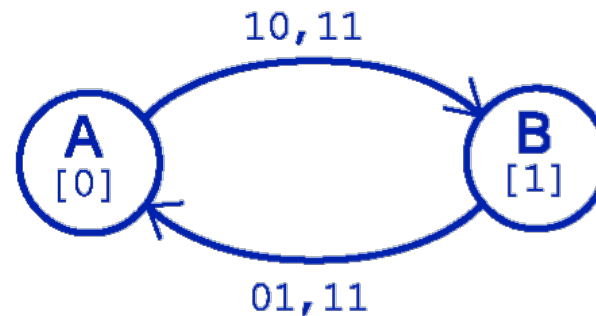

Different Implementations

- Although the behavior of Moore and Mealy machines is identical, their implementations differ:

Mealy machine

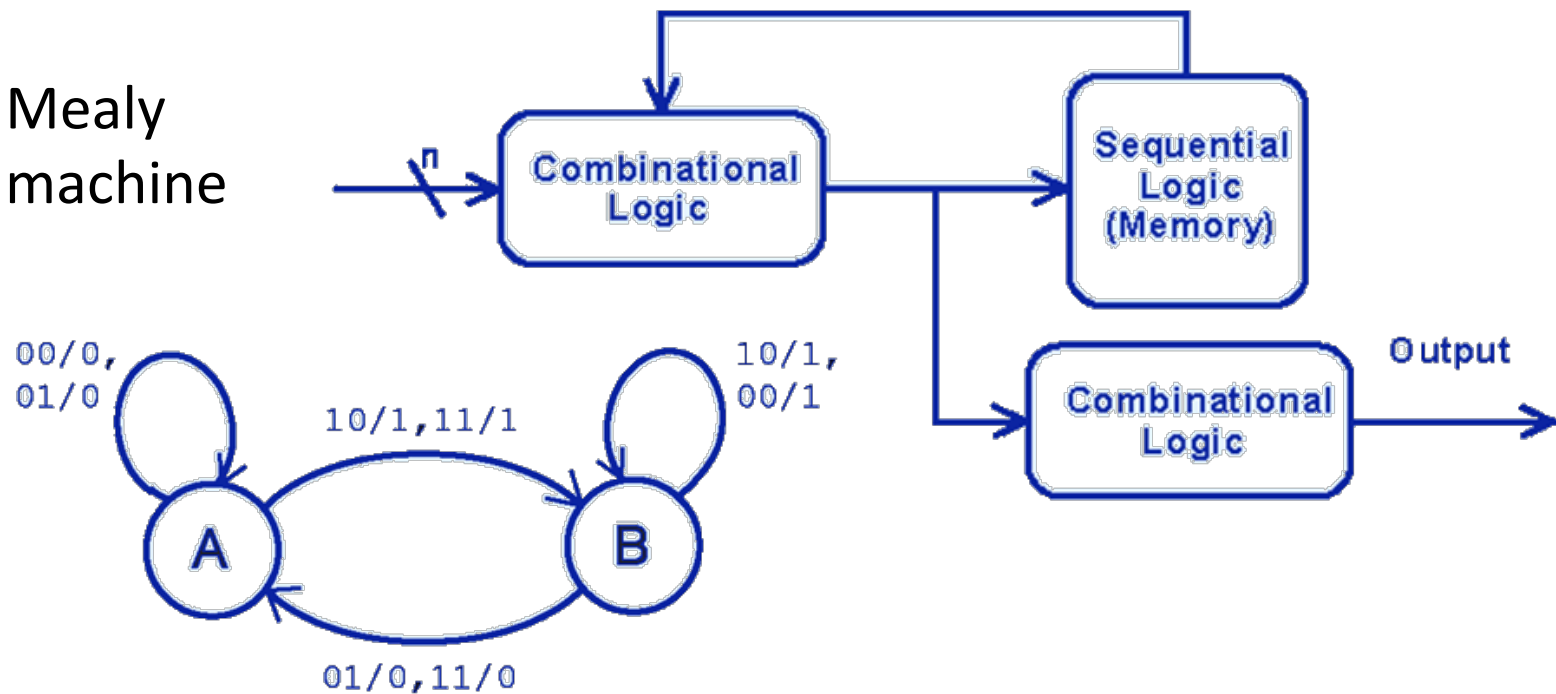


Algorithmic State Machine


- Moore and Mealy machines are challenging to draw for complex designs
 - An interaction of numerous signals is required to advance a machine from one state to the next
- Alternate approach: **Algorithmic State Machine**
 - A block diagram approach to describing digital systems

Algorithmic State Machine

State Block

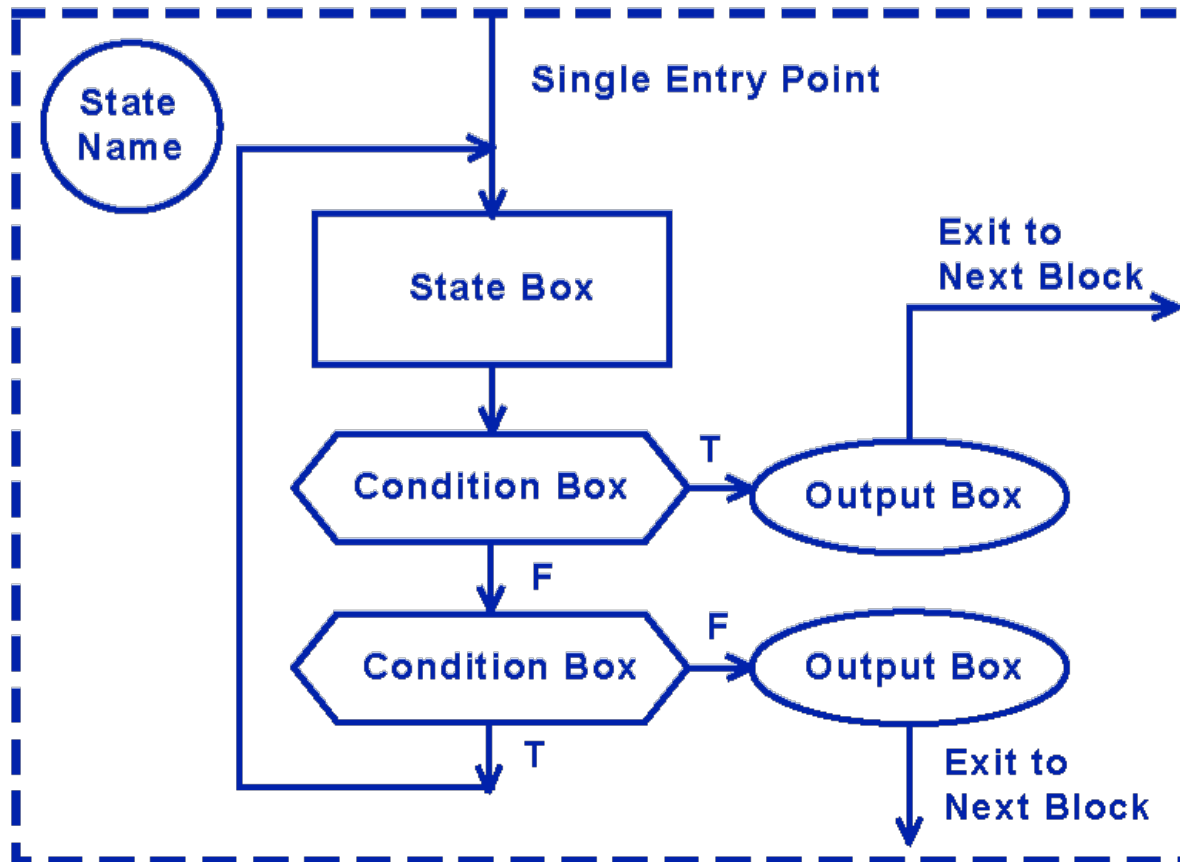

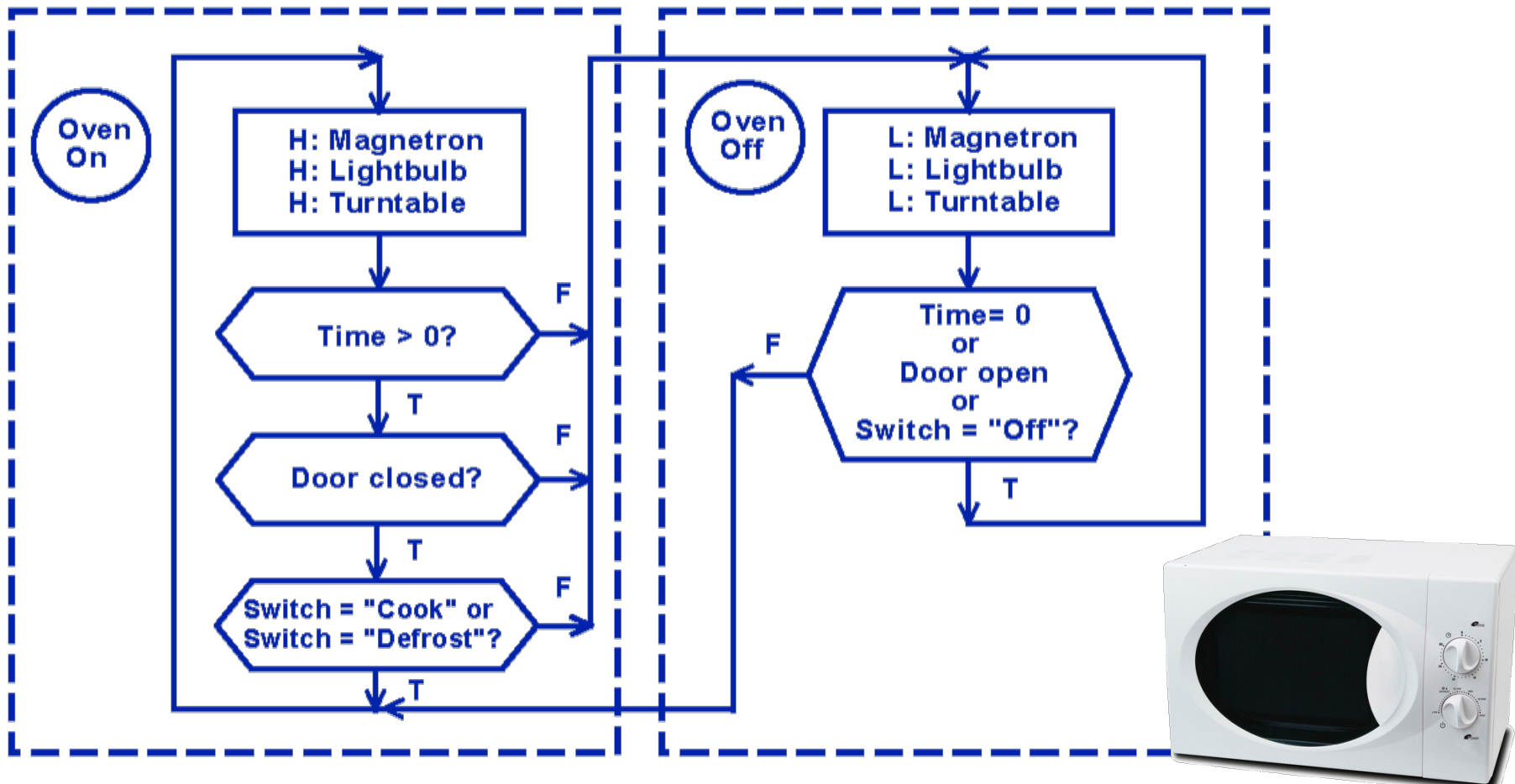Algorithmic State Machine – Microwave Oven




Sequential Circuit Applications


- When do I use sequential circuits?
 - Whenever the application is “**stateful**”
 - The next state of the machine depends on the **current state** of the machine and the input
- Stateful applications requires both combinational and sequential logic
- Examples: Register, Memory, Counters, ...

Sequential Circuits – Register

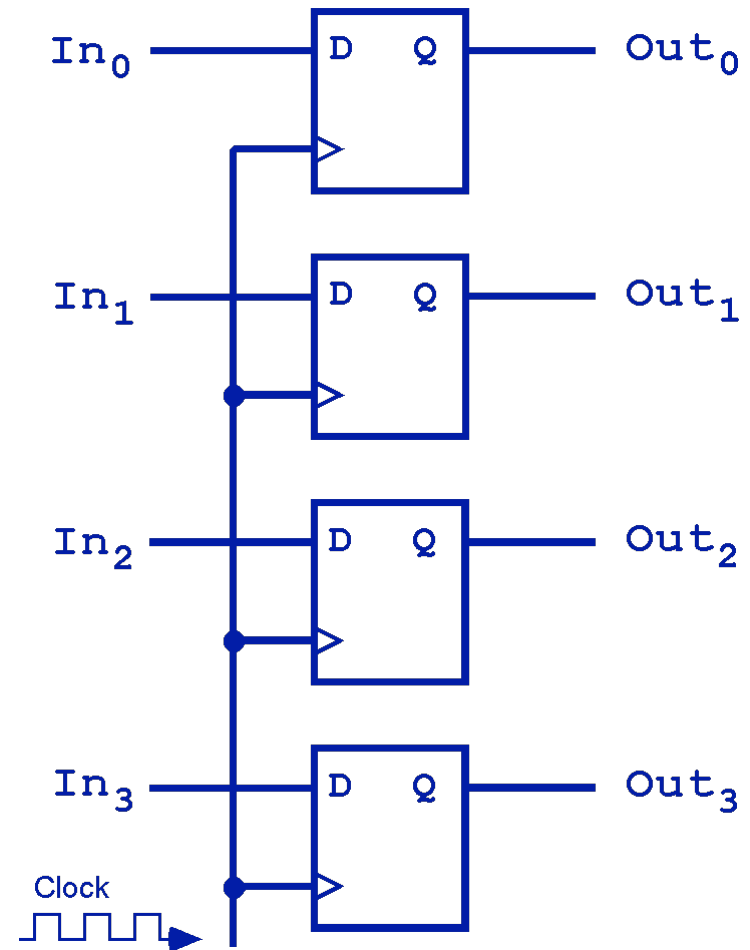➔ This illustration shows a 4-bit register consisting of D flip-flops. You will usually see its block diagram (below) instead.




Sequential Circuits – Group of Registers

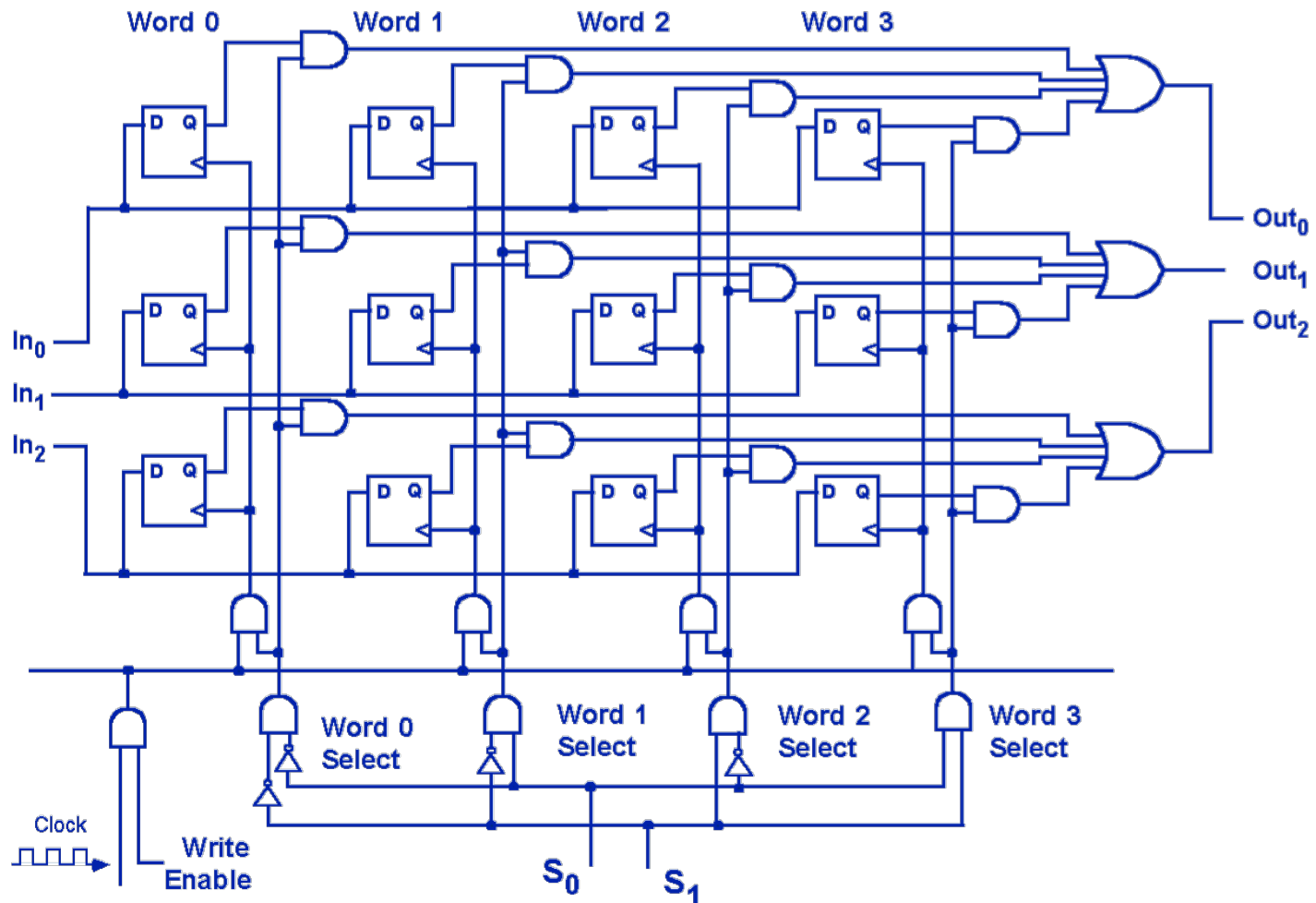

Sequential Circuits – Binary Counter

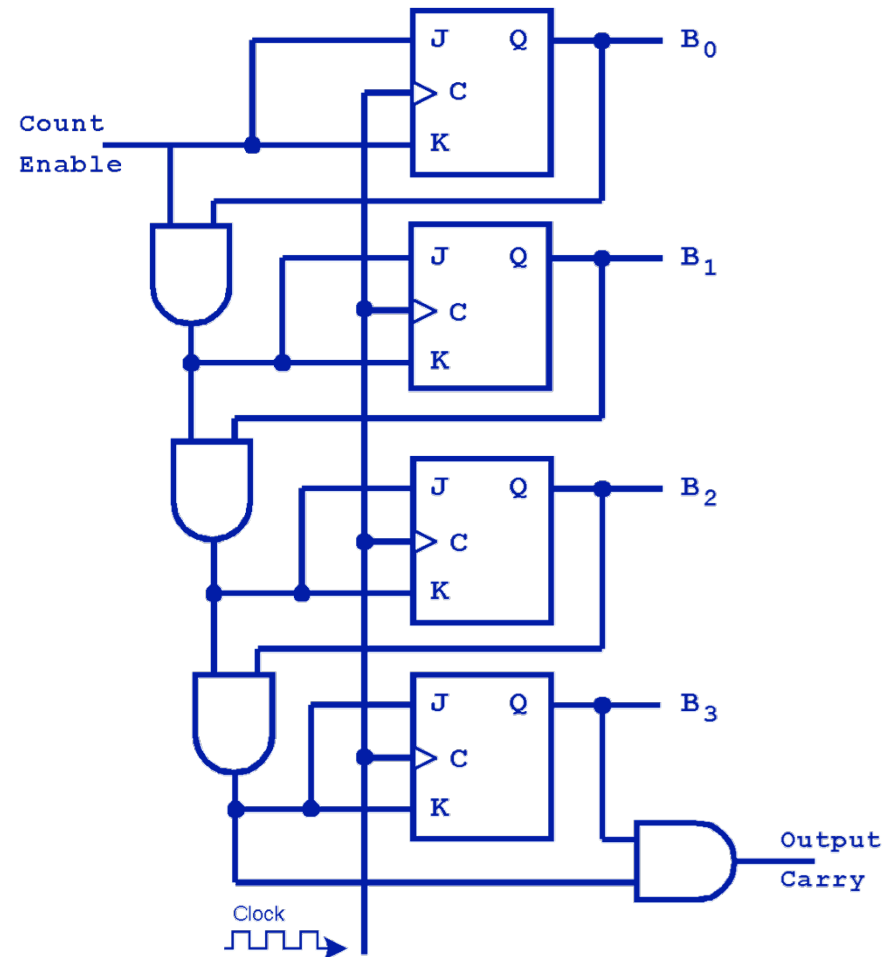- Binary counter operation
 - JK flip-flops toggle when $J=K=1$
 - Low-order bit is complemented at each clock pulse
 - Whenever low order bit changes from 0 to 1, the next bit is complemented, and so on through the other flip-flops



Designing Circuits

- **Do designers usually lay out circuits by hand?**
 - No – designers today rely on specialized software to create efficient circuits
 - Software is an enabler for the construction of better hardware!

- Many challenges in modern hardware designs
 - Sheer number of gates to implement!
 - Create “building blocks” (modules) that can be quickly assembled
 - Timing constraints – Result is **correct**, but **when** is it correct?
 - Propagation delays occur between the time when a circuit’s inputs are energized and when the output is accurate and stable

K-Maps



Introduction to Karnaugh Maps

- **Chapter 3A in textbook**
- Simplification of Boolean functions is good...
 - Produces simpler (and usually faster) digital circuits
- ... but also time-consuming and error-prone
 - Easy to mis-use identities

Introduction to Karnaugh Maps

- K-Maps are an easy, systematic method for reducing Boolean expressions
 - Named after Maurice Karnaugh (engineer at Bell Labs in 1950's)
 - Invented a graphical way of visualizing and then simplifying Boolean expressions

Introduction to Karnaugh Maps

- A Kmap is a matrix representing a Boolean function
 - Rows and column headers represent the input values
 - Cells represent corresponding output values
- Input values are formatted as *minterms*
 - Minterm is a product term that contains all of the function's variables exactly once, either complemented or not complemented

Minterms

➤ For example, the minterms for a function having the inputs x and y are: $\bar{x}\bar{y}$, $\bar{x}y$, $x\bar{y}$, and xy

➤ Consider the Boolean function,

➤ Its minterms are: $F(x, y) = xy + x\bar{y}$

Minterm	X	Y
$\bar{x}\bar{y}$	0	0
$\bar{x}y$	0	1
$x\bar{y}$	1	0
xy	1	1

Minterms

- Function with three inputs?
 - Minterms are similar...
 - Just imagine counting in binary to find all the minterms...

Minterm	X	Y	Z
$\bar{X}\bar{Y}\bar{Z}$	0	0	0
$\bar{X}\bar{Y}Z$	0	0	1
$\bar{X}Y\bar{Z}$	0	1	0
$\bar{X}YZ$	0	1	1
$X\bar{Y}\bar{Z}$	1	0	0
$X\bar{Y}Z$	1	0	1
$XY\bar{Z}$	1	1	0
XYZ	1	1	1

Introduction to Karnaugh Maps

- A Kmap has a cell for each minterm
 - Cell for each line for the truth table of a function
- The truth table for the function $F(x,y) = xy$ is shown along with its corresponding Kmap

$$F(X, Y) = XY$$

X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

		Y	
		0	1
X	0	0	0
	1	0	1

Introduction to Karnaugh Maps

- Truth table and Kmap for the function $F(x,y) = x + y$
- This function is equivalent to the OR of all of the minterms that have a value of 1

$$F(X, Y) = X + Y$$

X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

$$F(x, y) = x + y = \bar{x}y + x\bar{y} + xy$$

X \ Y	0	1
	0	0
1	1	1

Introduction to Karnaugh Maps

- Minterm function derived from Kmap was not in simplest terms
- Use Kmap to reduce expression to simplest terms
 - Find **adjacent 1's** in the Kmap that can be collected into groups that are **powers of two**

Two groups in this example:

	Y	0	1
X	0	0	1
1	1	1	1

Introduction to Karnaugh Maps

- Selected groups shown below
 - Groups are powers of two
 - Overlapping is OK!

X \ Y	0	1
0	0	1
1	1	1

Rules for Simplification

- Groupings can contain only 1's; no 0's
- Groups can be formed only at right angles
 - Diagonal groups are not allowed
- The number of 1's in a group must be a power of 2
 - A single 1 is OK then, but not three 1's!
- Groups must be made as large as possible
 - Otherwise simplification is incomplete
- Groups can overlap
- Groups can wrap around the sides of the Kmap

Kmap – Three Variables

- Extend to three variables? Easy!
- Note that the values for the yz combination at the top of the matrix form a pattern that is not a normal binary sequence
 - **Each position can only differ by 1 variable**

		YZ			
		00	01	11	10
X	0	$\bar{X}\bar{Y}\bar{Z}$	$\bar{X}\bar{Y}Z$	$\bar{X}YZ$	$\bar{X}Y\bar{Z}$
	1	$X\bar{Y}\bar{Z}$	$X\bar{Y}Z$	XYZ	$XY\bar{Z}$

Kmap – Three Variables

- What do the values look like?
 - First row contains all minterms where x has a value of zero.
 - First column contains all minterms where y and z both have a value of zero

		YZ			
		00	01	11	10
X	0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$\bar{x}yz$	$\bar{x}y\bar{z}$
	1	$x\bar{y}\bar{z}$	$x\bar{y}z$	xyz	$xy\bar{z}$

Kmap – Three Variables

➤ Example:

$$F(X, Y, Z) = \bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XYZ$$

➤ Kmap:

X \ YZ	00	01	11	10
0	0	1	1	0
1	0	1	1	0

➤ What is the largest group of 1's that is a power of 2?

Kmap – Three Variables

- Look at the grouping closely
 - Changes in the variables x and y have no influence upon the value of the function
 - Thus, the function

$$F(X, Y) = \bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XYZ$$

- reduces to $F(x) = z$

You could verify this reduction with identities or a truth table

		YZ			
		00	01	11	10
X	0	0	1	1	0
	1	0	1	1	0

Kmap – Three Variables

➤ Example:

$$F(X, Y, Z) = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}YZ + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z}$$

➤ Kmap:

X \ YZ	00	01	11	10
0	1	1	1	1
1	1	0	0	1

➤ **What are the largest groups of 1's that are a power of 2?**

➤ **How many groups do you see?**

Kmap – Three Variables

- To make the **largest groups possible**, wrap around the sides
- **How do we interpret results?**
 - Green row?
 - Pink square?

	YZ	00	01	11	10
x	0	1	1	1	1
1	1	1	0	0	1

The Karnaugh map shows a green row highlighting the top row (x=0) and a pink square highlighting the four corners (x=0, yz=00 and 10; x=1, yz=00 and 10). A yellow background highlights the entire map area.

Kmap – Three Variables

- Green group – only the value of x is significant
 - Thus, \bar{X}
- Pink group – only the value of z is significant
- Our reduced function is: $F(X, Y, Z) = \bar{X} + \bar{Z}$

Recall that we had six minterms in our original function!

	YZ	00	01	11	10
X	0	1	1	1	1
1	1	1	0	0	1

Kmap – Four Variables

- Model can be extended to accommodate a four-input function
 - 16 minterms produced

		YZ			
		00	01	11	10
WX	00	$\bar{W}\bar{X}\bar{Y}\bar{Z}$	$\bar{W}\bar{X}\bar{Y}Z$	$\bar{W}\bar{X}YZ$	$\bar{W}\bar{X}Y\bar{Z}$
	01	$\bar{W}X\bar{Y}\bar{Z}$	$\bar{W}X\bar{Y}Z$	$\bar{W}XYZ$	$\bar{W}XY\bar{Z}$
	11	$WX\bar{Y}\bar{Z}$	$WX\bar{Y}Z$	$WXYZ$	$WXY\bar{Z}$
	10	$W\bar{X}\bar{Y}\bar{Z}$	$W\bar{X}\bar{Y}Z$	$W\bar{X}YZ$	$W\bar{X}Y\bar{Z}$

Kmap – Four Variables

➤ Example:
$$F(W, X, Y, Z) = \bar{W}\bar{X}\bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Y}Z + \bar{W}\bar{X}Y\bar{Z} + \bar{W}\bar{X}YZ + W\bar{X}\bar{Y}\bar{Z} + W\bar{X}\bar{Y}Z + W\bar{X}Y\bar{Z} + W\bar{X}YZ$$

➤ Kmap (showing non-zero terms)

➤ **What largest groups should we select?**

➤ Groups can overlap!

➤ Groups can wrap!

		YZ			
		00	01	11	10
WX	00	1	1		1
	01				1
	11				
	10	1	1		1

Kmap – Four Variables

➤ Three groups

1. Pink group that wraps top and bottom
2. Green group that spans the corners
3. Purple group entirely within the Kmap at the right

WX \ YZ	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

The Kmap shows three groups of 1s: a pink group wrapping from the top row (WX=00) to the bottom row (WX=10) for YZ=00 and 01; a green group spanning the corners (WX=00, YZ=10) and (WX=10, YZ=10); and a purple group in the right column (YZ=10) for WX=00 and 01.

$$F(W, X, Y, Z) = \bar{X}\bar{Y} + \bar{X}\bar{Z} + \bar{W}Y\bar{Z}$$

Kmap – Four Variables

- Kmap simplification may not be unique
 - Possible to have different largest possible groups...
- The (different) functions that result from the groupings below are logically equivalent

		YZ			
		00	01	11	10
WX	00	1		1	
	01	1		1	1
	11	1			
	10	1			

Groupings in the first Kmap: a vertical green group (WX 00, 01, 11, 10; YZ 00), a vertical blue group (WX 00, 01; YZ 11), and a horizontal pink group (WX 01; YZ 00, 01, 10).

		YZ			
		00	01	11	10
WX	00	1		1	
	01	1		1	1
	11	1			
	10	1			

Groupings in the second Kmap: a vertical blue group (WX 00, 01, 11, 10; YZ 00), a vertical green group (WX 00, 01; YZ 11), and a horizontal pink group (WX 01; YZ 11, 10).

Don't Care Conditions



- Real circuits don't always need to have an output defined for every possible input
 - Example: Calculator displays have 7-segment LEDs. These LEDs can display 2^7-1 patterns, but only ten of them are useful
- If a circuit is designed so that a particular set of inputs can never happen, we call this set of inputs a don't care condition
 - Helpful for Kmap circuit simplification

Don't Care Conditions

- Represent a don't care condition with an X
- Free to include or ignore the X's when choosing groups

WX \ YZ	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

Don't Care Conditions

➤ Grouping option #1:

		YZ			
		00	01	11	10
WX	00	X	1	1	X
	01		X	1	
	11	X		1	
	10			1	
				1	

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

Don't Care Conditions

➤ Grouping option #2:

		YZ			
		00	01	11	10
WX	00	X	1	1	X
	01		X	1	
	11	X		1	
	10			1	
				1	

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$

Don't Care Conditions

➤ The truth table of

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

➤ differs from the truth table of

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$

➤ However, the values for which they differ are the inputs for which we have don't care conditions

➤ **Either is an acceptable solution**

Homework #1 Review

- **Grades and solutions** posted on **Sakai**
 - Papers available after class (for those with Sakai issues...)
- 50-word sentence - **Describe why the “Von Neumann bottleneck” constrains CPU performance**
 - *The Von Neumann Bottleneck is a constraint on stored program machines in which the computer is limited to a single path between the main memory and the CPU, which forces the CPU to alternate between fetching and processing data, thereby limiting efficiency and performance.*
 - 44 words (< 50 word limit), 1 sentence

Quiz #1 Review

- **Grades and solutions** posted on Sakai
- Problem 4 - **Why were transistors a huge technology improvement over vacuum tubes?**
 - Cooler, more reliable, cheaper, smaller, faster, ...
- Problem 5 - **What does Moore's Law "promise"?**
As of 2011, is the law still in effect?
 - Number of transistors you can buy (for fixed \$\$ / size) doubles ~2 years
 - Not "performance"!

Quiz #1 Review

- Problem 6 - **Memory is large and contains many instructions and data. How does the hardware know which instruction should be executed next?**
 - Program counter has next address in memory
- Problem 6 - **What function does the ALU perform?**
 - Mathematical operations! (Add, sub, mul, div, compare, ...)