



Computer Systems and Networks

ECPE 170 – Jeff Shafer – University of the Pacific

Digital Logic Sequential Circuits

Quiz 1

↗ Return Quiz 1 and review

Upcoming Events

➤ Quiz 2 – Friday Feb 3rd

➤ Topics *may or may not* include:

- Simplifying Boolean expressions with identities
- Converting between a truth table and a circuit diagram (with logic gates)
- Common combinational circuits: adders, decoders, multiplexers, shifters
 - Basic operation of these devices, i.e. inputs and outputs
- Sequential circuits: SR, JK, D flip-flops
 - Basic operation of these devices, i.e. inputs and outputs

Recap from Last Class

- **Why do real hardware devices use NAND / NOR gates instead of AND / OR / NOT gates?**
 - These are “universal” gates – any function can be made using only NAND or only NOR gates
 - Simplifies manufacturing to use the same gate type

Recap from Last Class


- **What is a combinational circuit?**
 - Circuit where output is based on input only

Recap from Last Class

- **What is the difference between a half-adder and a full-adder?**
 - **Half adder** adds two inputs (x , y) and produces sum and carry-out
 - **Full adder** adds three inputs (x , y , carry-in) and produces sum and carry-out
 - We build it out of two half-adders!


Combinational Circuit – Multiplexer

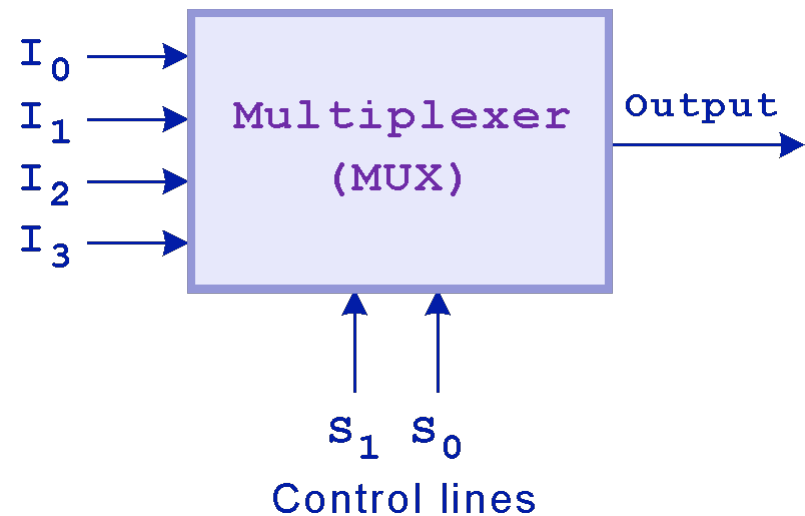- A **multiplexer** selects a single output from several inputs
- Which input is chosen?
 - Selected by the value on the multiplexer's control lines
- To select from n inputs, $\log_2 n$ control lines are needed.



Combinational Circuit – Multiplexer


➔ Implementation of a 4-to-1 multiplexer

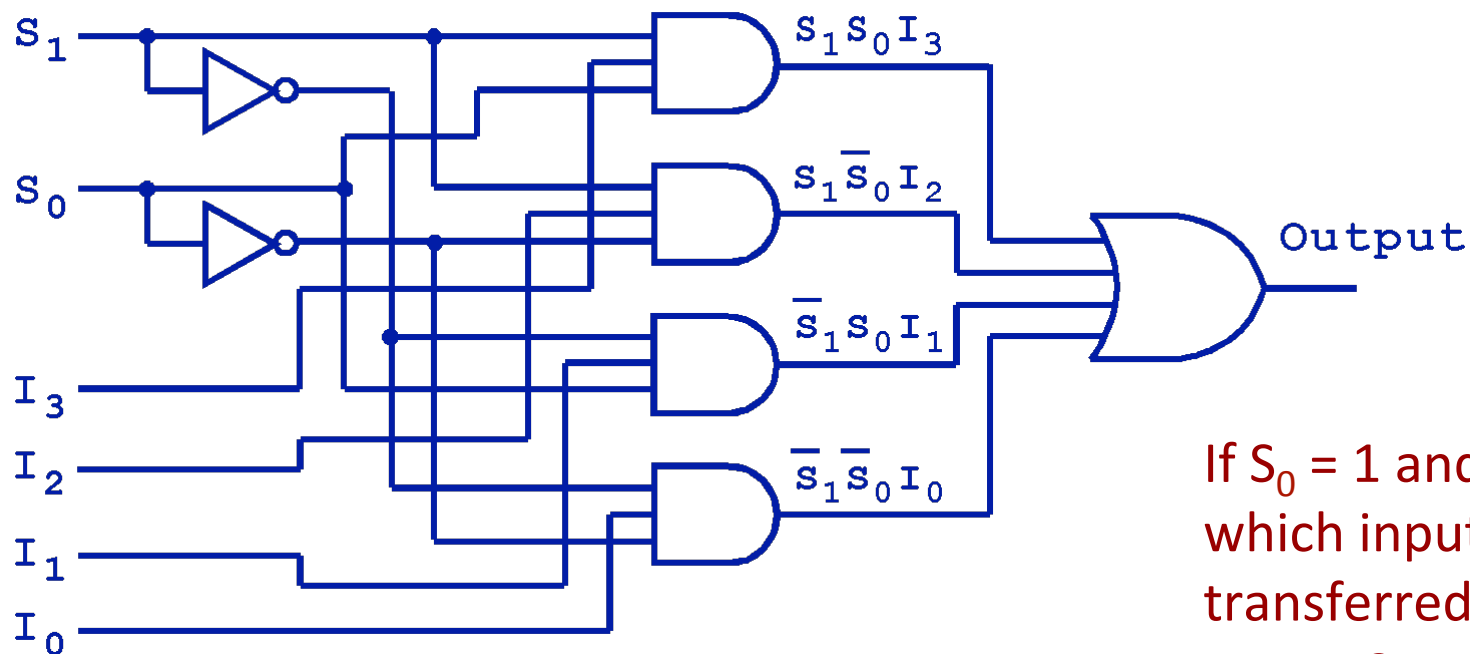

If $S_0 = 1$ and $S_1 = 0$,
which input is
transferred to the
output?

Combinational Circuit – Shifter

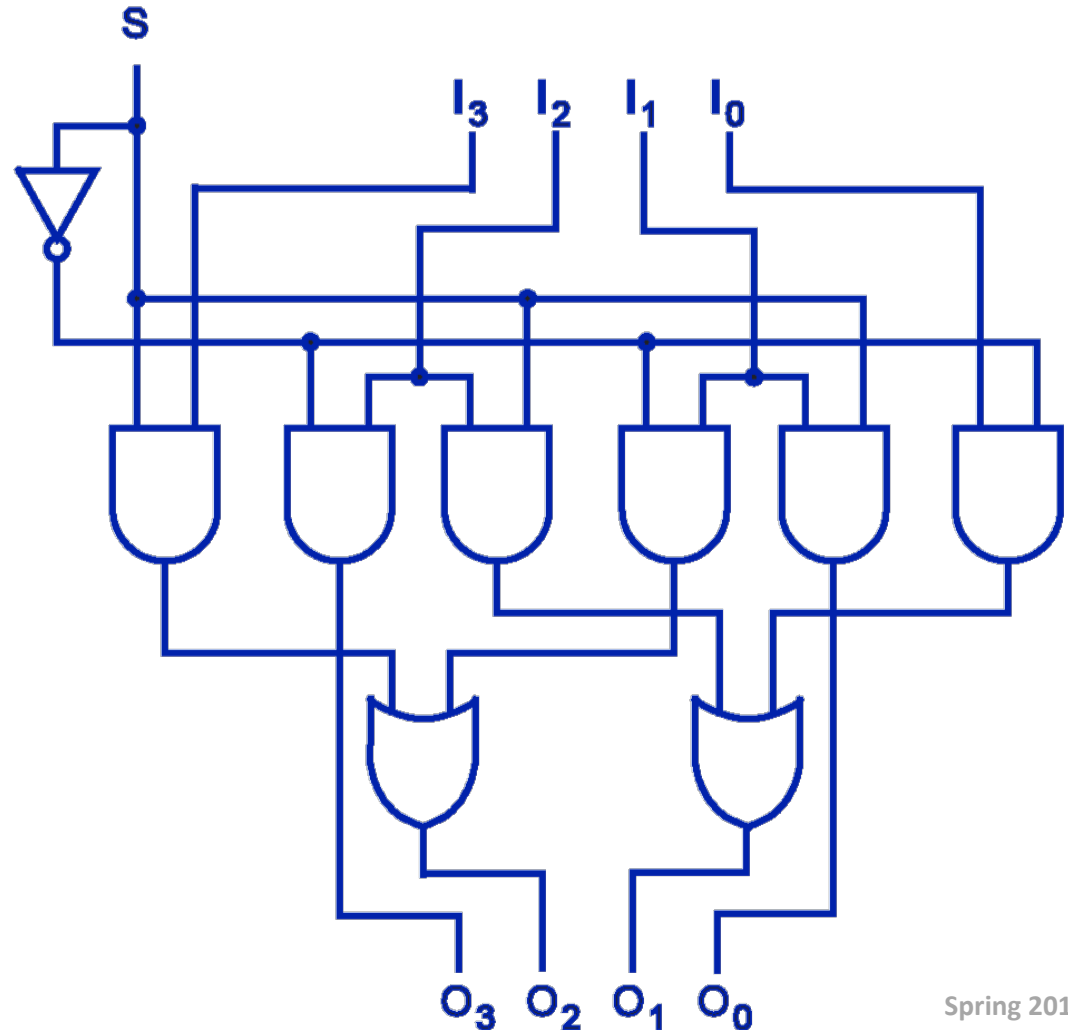- This **shifter** moves the bits of a 4-bit input one position to the left or right
- **If $S = 0$, in which direction do the input bits shift?**
- Left!



Combinational Circuits

- **Does the output of a combinational circuit change instantly when the input changes?**
 - No – takes a tiny (but measurable) length of time
 - Electrical signals in a wire have a finite speed
 - A transistor takes a finite time to change state

Sequential Circuits




Sequential Circuits

- Combinational logic circuits
 - Immediately apply Boolean function to set of inputs
 - This does not work for all problems!

- What if we want a circuit that changes its value based on (a) its **inputs** and (b) its **current state**?
 - These circuits have to “remember” their current state
 - This is a **sequential logic circuit**


Sequential Circuits

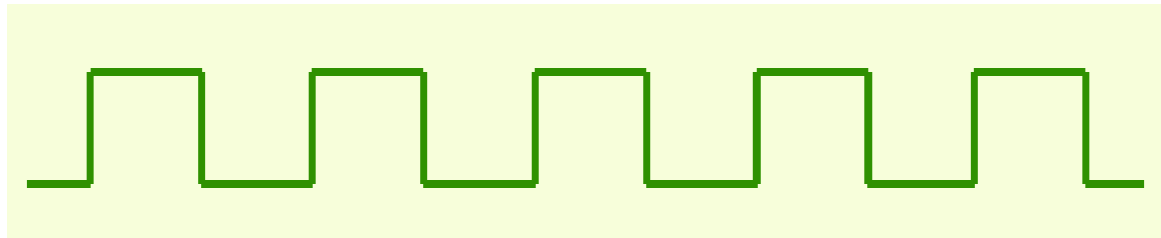- Sequential logic circuits require a means by which events can be sequenced
 - The **clock**!
- What is a clock?
 - Not a “wall clock”
 - Circuit that sends electrical pulses through a system




Sequential Circuits

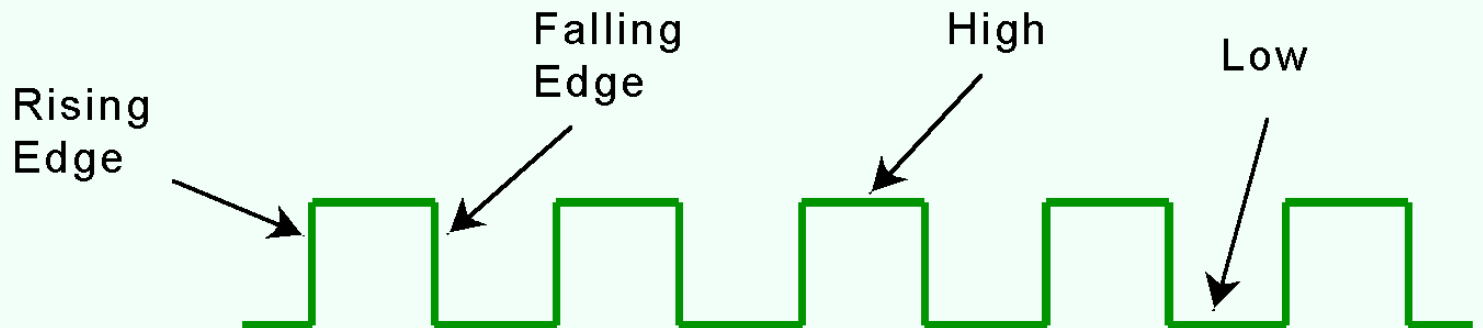- State changes occur in sequential circuits only when the clock “ticks”
- Circuits can change state on the:
 - Rising edge, or
 - Falling edge, or *Pick 1 option, not all 3!*
 - When the clock pulse reaches its highest voltage




Sequential Circuits

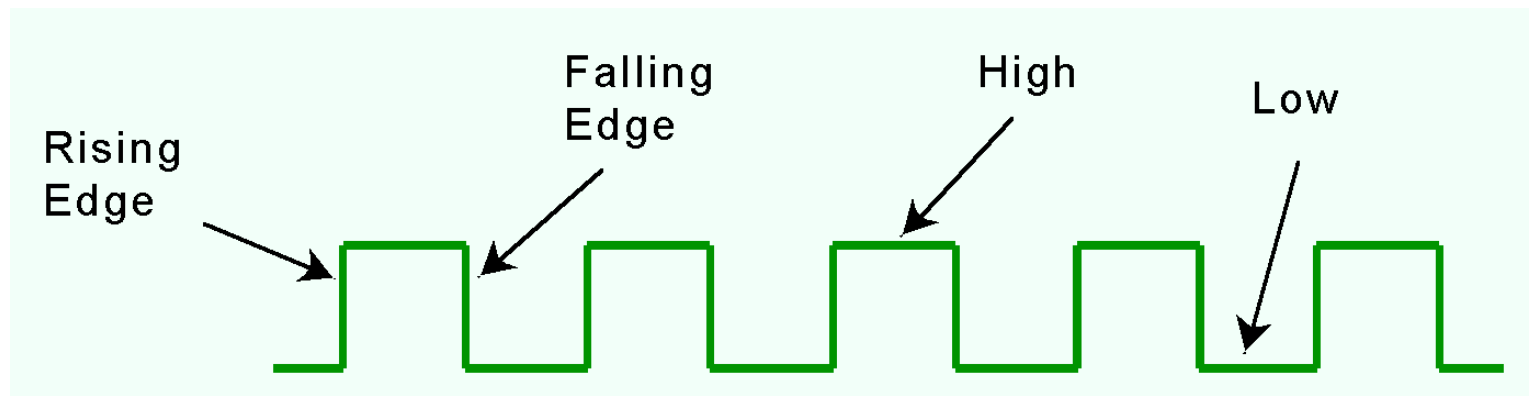- **Edge-triggered** circuits
 - Change state on the rising edge or falling edge of the clock pulse
- **Level-triggered** circuits
 - Change state when the clock voltage reaches its highest or lowest level



Sequential Circuits

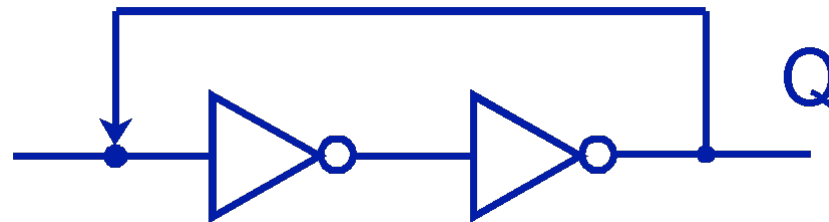
- **How can we make a circuit that uses its current output in deciding its next output?**
 - Feedback – loop an output back to the input
- Example:
 - If Q is 0 it will always be 0
 - If Q is 1, it will always be 1




Sequential Circuits – SR Flip-flop

- SR Flip-flop employs feedback
 - The “SR” stands for set/reset
 - Basic storage element

Internal design (clock not shown):

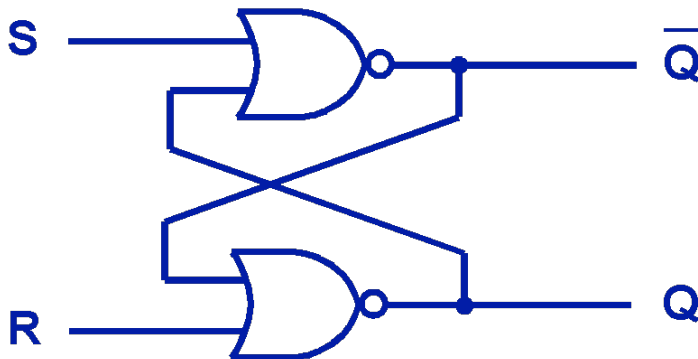


Block diagram (with clock):

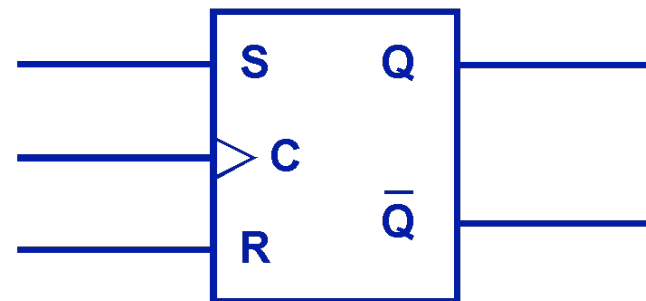

Sequential Circuits – SR Flip-flop

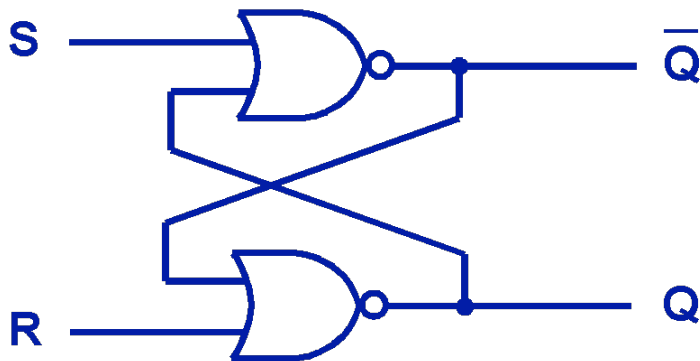- What does the truth table of an SR flip-flop look like?
 - $Q(t)$ is the value of the output Q at time t
 - $Q(t+1)$ is the value of Q after the next clock pulse



S	R	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	undefined


Sequential Circuits – SR Flip-flop

- The SR flip-flop actually has three inputs: S, R, and its current output, Q
- More complete truth table
 - Two undefined values!
 - SR flip-flop unstable when “set” and “reset” are both active

Present State			Next State
S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	undefined
1	1	1	undefined


Sequential Circuits – JK Flip-flop

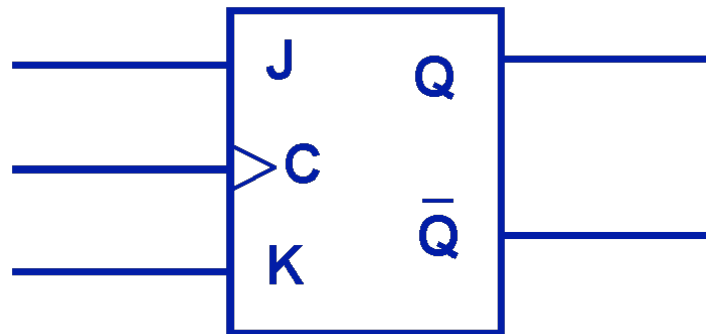- **JK flip-flop** removes this risk
 - Ensures that both “set” and “reset” inputs to an SR flip-flop will never both be 1
 - “JK” named after Jack Kilby
 - 2000 Nobel Prize winner for invention of the integrated circuit while at Texas Instruments



Sequential Circuits – JK Flip-flop

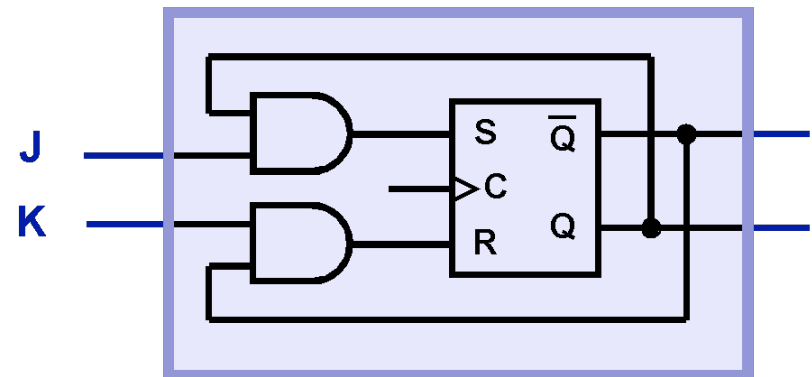
- JK flip-flop is really just a wrapper around a basic SR flip-flop
- JK is stable for all inputs
 - J=K=1: Toggle output



J	K	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$

Sequential Circuits – D Flip-flop

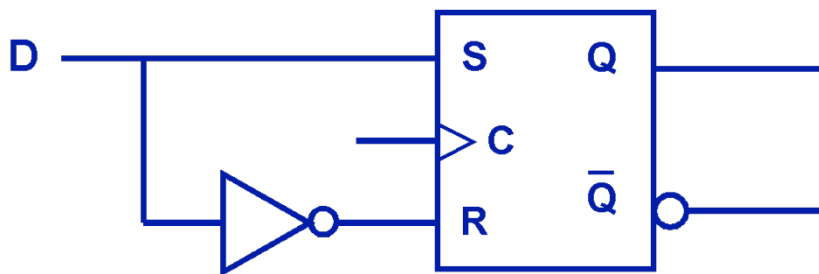
- D Flip-Flop
 - Another modification of the SR flip-flop
 - $D = \text{Data}$ (*but I remember $D = \text{Delay}$...*)
- Output of the flip-flop remains the same during subsequent clock pulses
 - Output changes only when D changes



D	$Q(t+1)$
0	0
1	1

Sequential Circuits – D Flip-flop

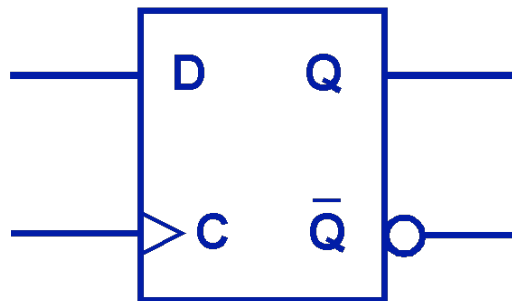- D flip-flop is the fundamental circuit of computer memory
 - Usually illustrated using the block diagram shown below



D	$Q(t+1)$
0	0
1	1

State Machines




State Machines

- How do we design complicated sequential systems?
 - **Finite State Machine (FSM)**
 - In visual form
 - A set of nodes that hold the states of the machine
 - A set of arcs that connect the states


- Two different types of state machines: **Moore** and **Mealy**
 - Both produce systems that produce the same output
 - Differ only in how the output of the machines are expressed
 - Moore: place outputs on each node
 - Mealy: present outputs on the transitions

JK Flip-Flop in State Machine Form

Moore FSM

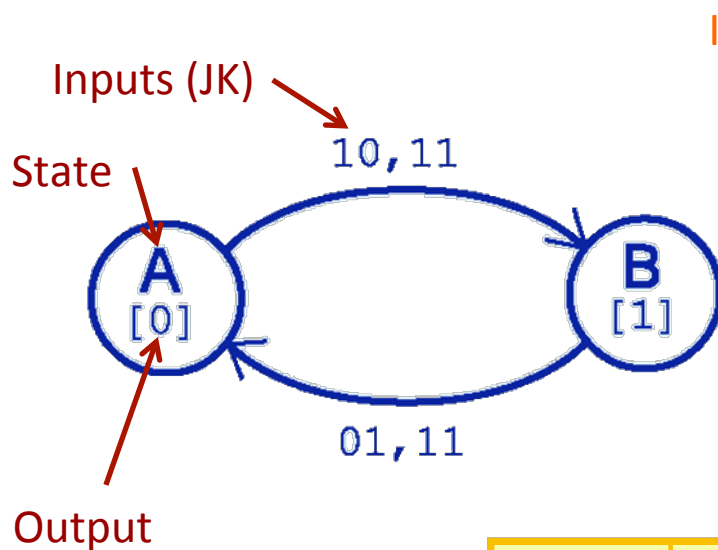

Mealy FSM


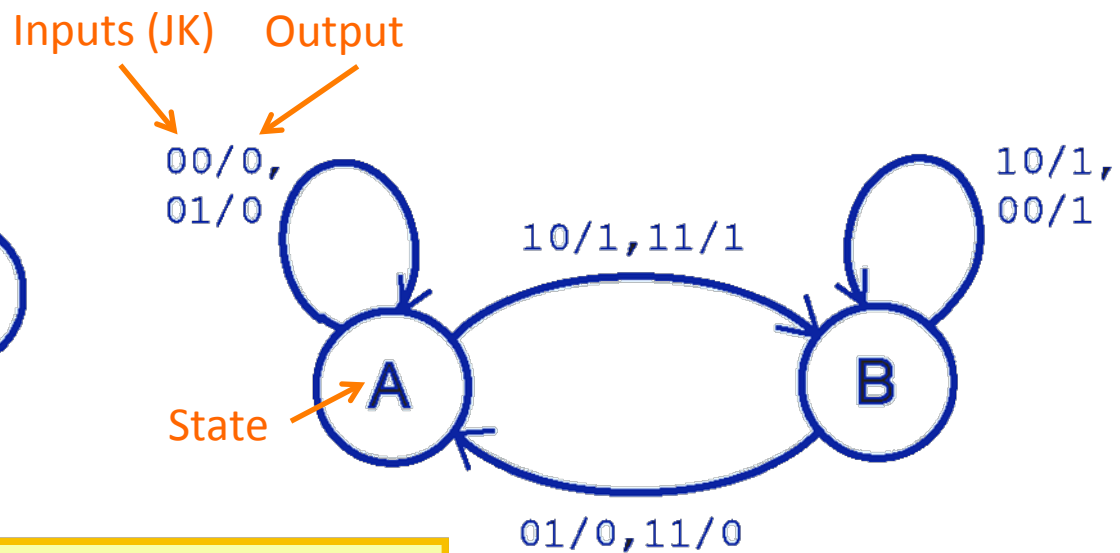


J	K	Q(t+1)
0	0	Q(t) (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$

Different Implementations

- Although the behavior of Moore and Mealy machines is identical, their implementations differ:


Moore machine:

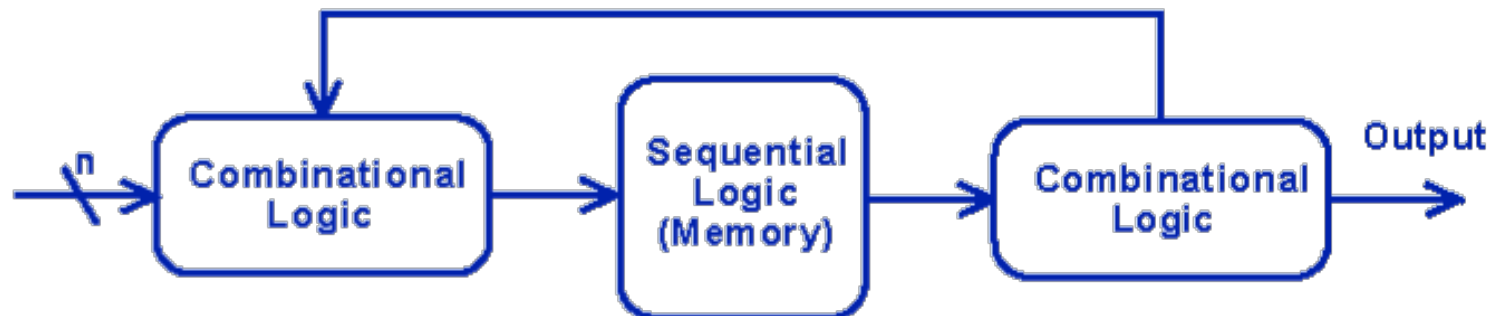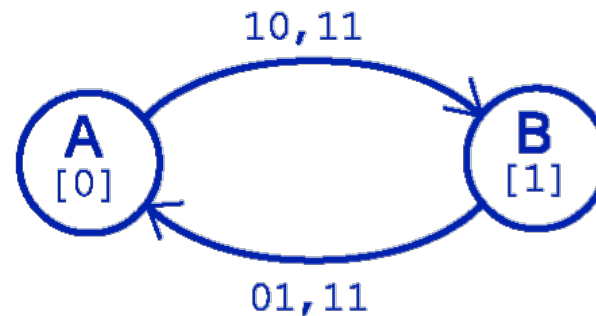

Different Implementations

- Although the behavior of Moore and Mealy machines is identical, their implementations differ:

Mealy machine

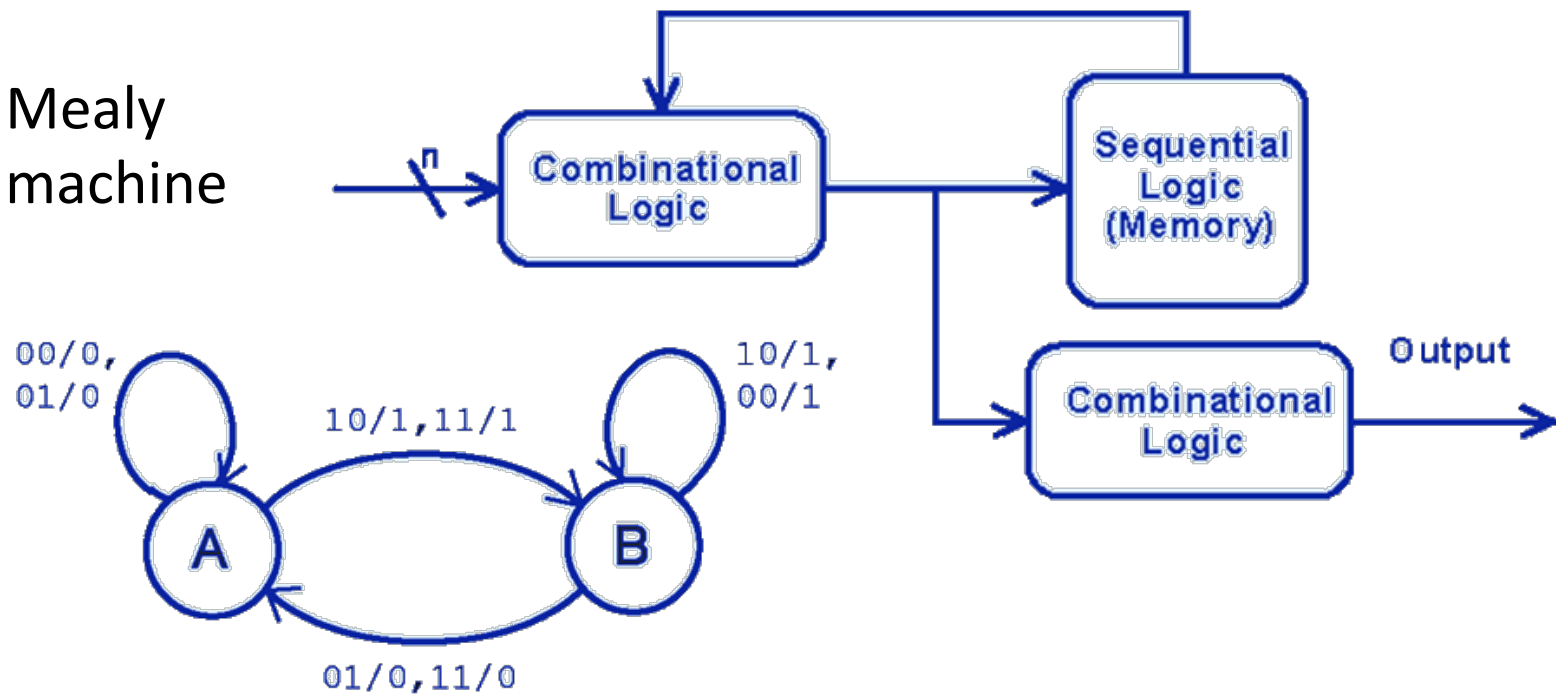


Sequential Circuit Applications


- When do I use sequential circuits?
 - Whenever the application is “**stateful**”
 - The next state of the machine depends on the **current state** of the machine and the input
- Stateful applications requires both combinational and sequential logic
- Examples: Register, Memory, Counters, ...

Sequential Circuits – Register

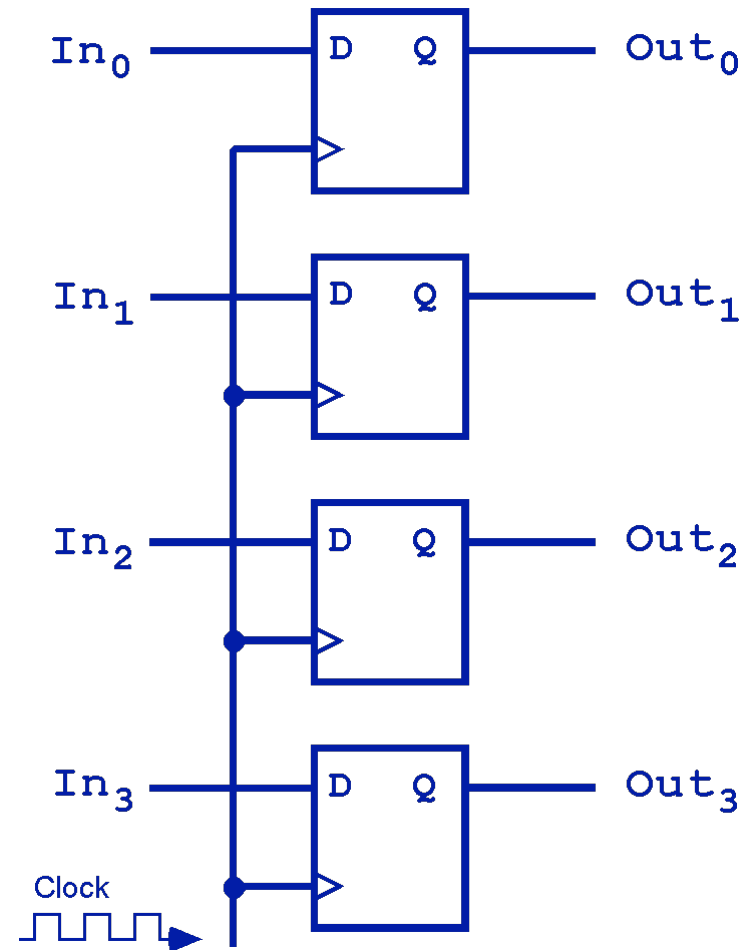➔ This illustration shows a 4-bit register consisting of D flip-flops. You will usually see its block diagram (below) instead.




Sequential Circuits – Group of Registers

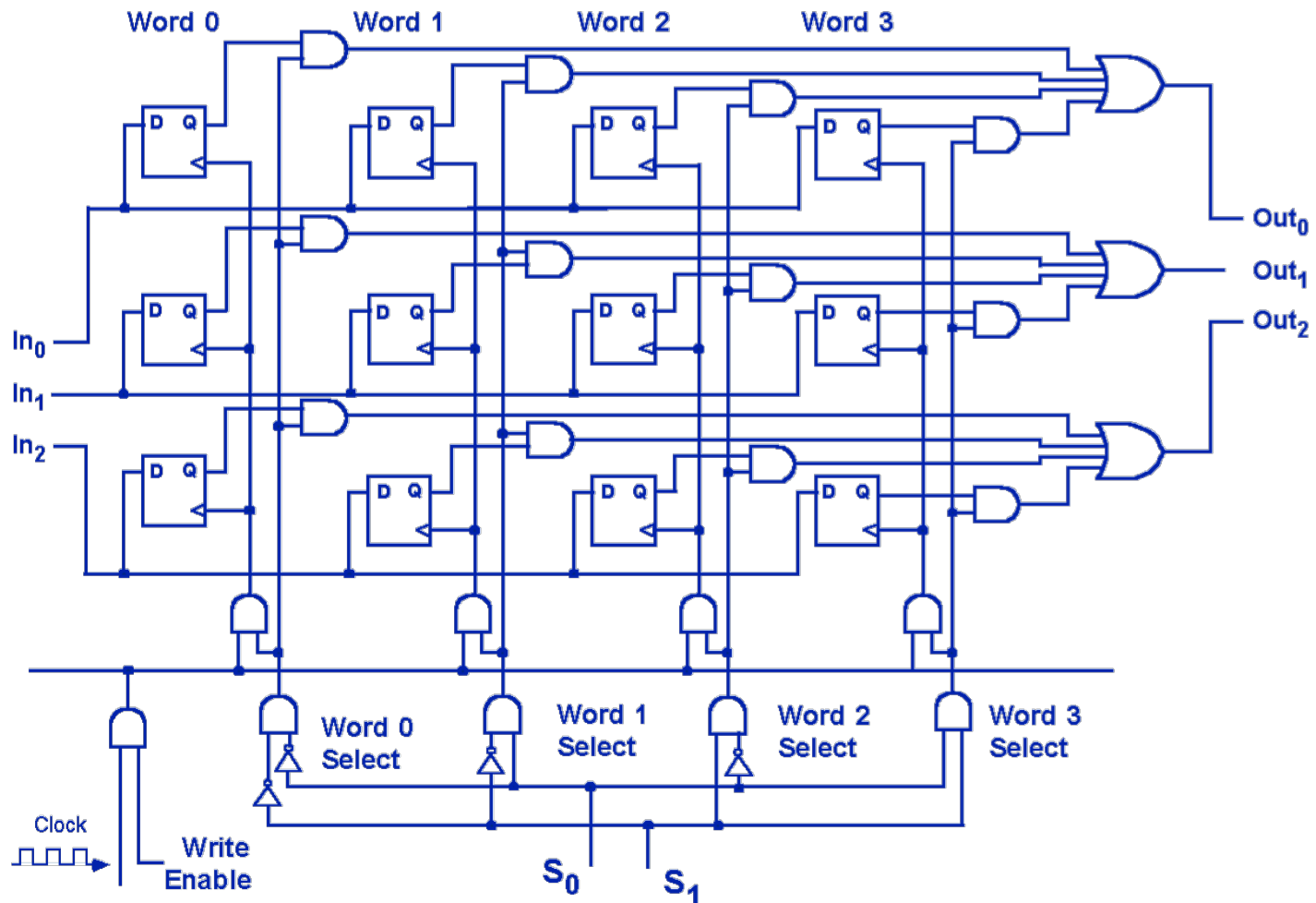

Sequential Circuits – Binary Counter

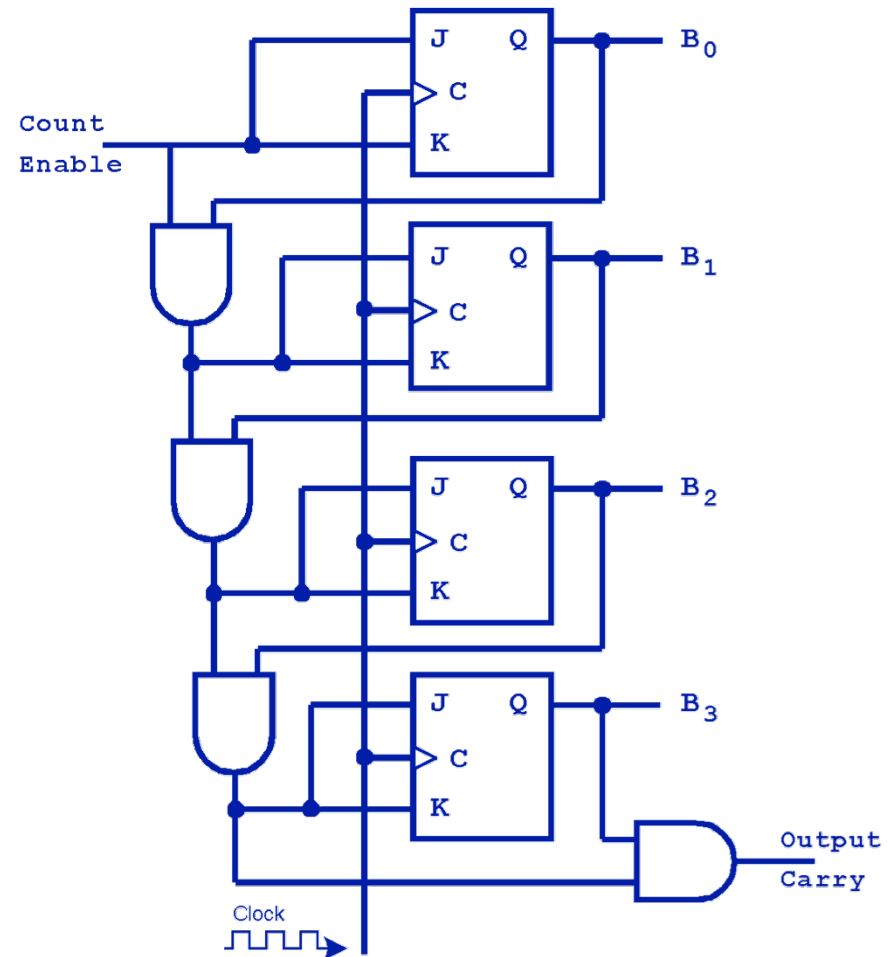- Binary counter operation
 - JK flip-flops toggle when $J=K=1$
 - Low-order bit is complemented at each clock pulse
 - Whenever low order bit changes from 0 to 1, the next bit is complemented, and so on through the other flip-flops



Designing Circuits

- **Do designers usually lay out circuits by hand?**
 - No – designers today rely on specialized software to create efficient circuits
 - Software is an enabler for the construction of better hardware!

- Many challenges in modern hardware designs
 - Sheer number of gates to implement!
 - Create “building blocks” (modules) that can be quickly assembled
 - Timing constraints – Result is **correct**, but **when** is it correct?
 - Propagation delays occur between the time when a circuit’s inputs are energized and when the output is accurate and stable

“Bonus” Slides

– Algorithmic State Machines




Algorithmic State Machine

- Moore and Mealy machines are challenging to draw for complex designs
 - An interaction of numerous signals is required to advance a machine from one state to the next
- Alternate approach: **Algorithmic State Machine**
 - A block diagram approach to describing digital systems

Algorithmic State Machine

State Block

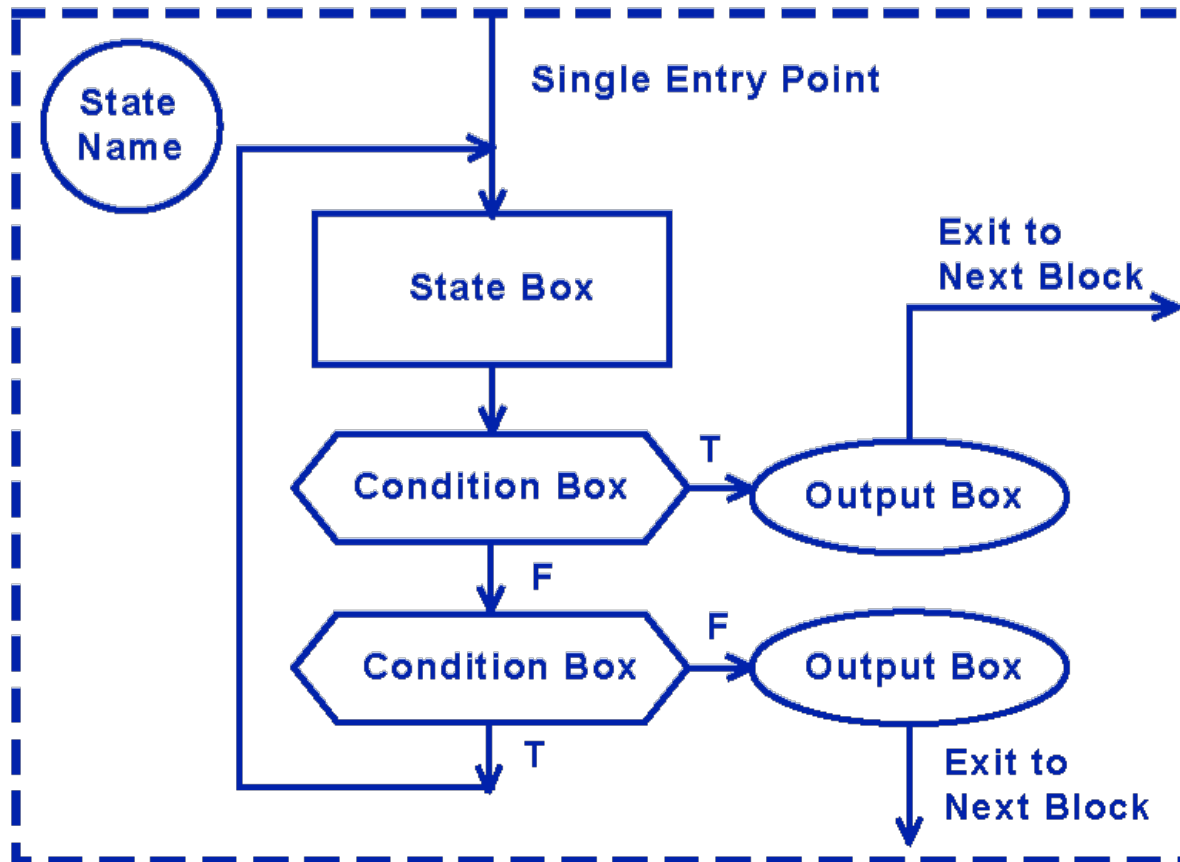

Algorithmic State Machine – Microwave Oven

