



# Computer Systems and Networks

ECPE 170 – Jeff Shafer – University of the Pacific


## Karnaugh Maps

# Schedule

- **Friday 3<sup>rd</sup> - Quiz 2**
  - Review K-maps and/or Simple computer organization
  
- **Monday 6<sup>th</sup>**
  - Simple computer organization
  - Exam review
  
- **Wednesday 8<sup>th</sup> - Exam 1**
  - *Will discuss later*
  - *Exam covers all of Chapters 2 and 3*
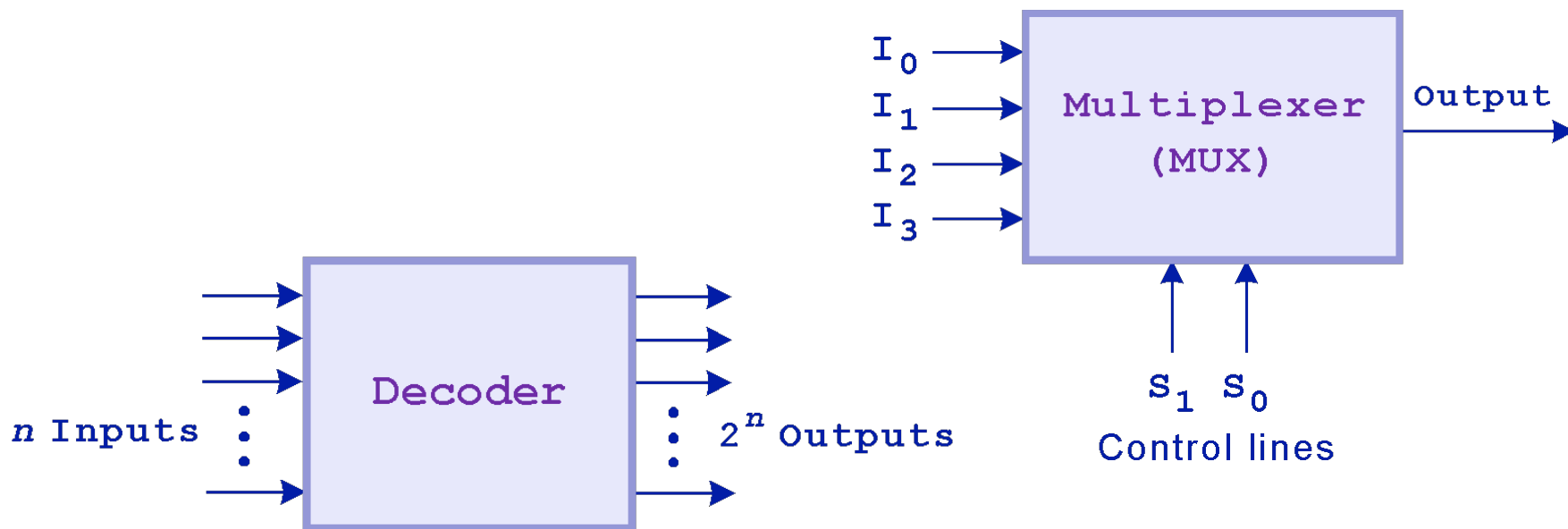
# Recap

➤ **What is the difference between a decoder and a multiplexer?**






# Recap

- **What is the clock of a digital circuit?**
- Square wave signal
- “Pulse” of a sequential circuit – allows events to happen in a sequence


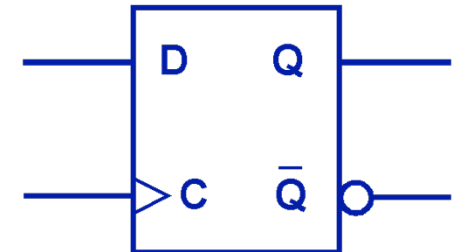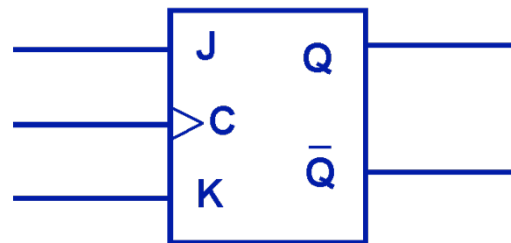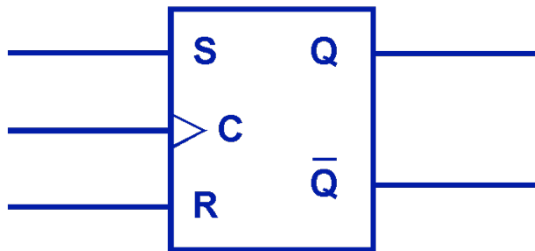
# Recap

➔ What are the outputs of these common flip-flops?  
(and what are their names?)



| S | R | $Q(t+1)$           |
|---|---|--------------------|
| 0 | 0 | $Q(t)$ (no change) |
| 0 | 1 | 0 (reset to 0)     |
| 1 | 0 | 1 (set to 1)       |
| 1 | 1 | undefined          |

| J | K | $Q(t+1)$           |
|---|---|--------------------|
| 0 | 0 | $Q(t)$ (no change) |
| 0 | 1 | 0 (reset to 0)     |
| 1 | 0 | 1 (set to 1)       |
| 1 | 1 | $\bar{Q}(t)$       |

| D | $Q(t+1)$ |
|---|----------|
| 0 | 0        |
| 1 | 1        |

# K-Maps



# Introduction to Karnaugh Maps

- **Chapter 3A in textbook**
- Simplification of Boolean functions is good...
  - Produces simpler (and usually faster) digital circuits
- ... but also time-consuming and error-prone
  - Easy to mis-use identities

# Introduction to Karnaugh Maps

- K-Maps are an easy, systematic method for reducing Boolean expressions
  - Named after Maurice Karnaugh (engineer at Bell Labs in 1950's)
  - Invented a graphical way of visualizing and then simplifying Boolean expressions



# Introduction to Karnaugh Maps

- A Kmap is a matrix representing a Boolean function
  - Rows and column headers represent the input values
  - Cells represent corresponding output values
- Input values are formatted as *minterms*
  - Minterm is a product term that contains all of the function's variables exactly once, either complemented or not complemented

# Disclaimer

- **WARNING:** Are you currently taking ECPE 71 this semester? (or have already taken it?)
  - **Do K-Maps the way Dr. Basha told you to!**
- Our book
  - Flips the axis ( $w$   $x$  on left,  $y$   $z$  on top)
  - Only cares about consolidating 1's, and thus doesn't always write in the 0's
- The answer is the same, so use whatever process you already know

# Minterms

➤ For example, the minterms for a function having the inputs  $x$  and  $y$  are:  $\bar{x}\bar{y}$ ,  $\bar{x}y$ ,  $x\bar{y}$ , and  $xy$

➤ Consider the Boolean function,

➤ Its minterms are:  $F(x, y) = xy + x\bar{y}$

| Minterm          | X | Y |
|------------------|---|---|
| $\bar{x}\bar{y}$ | 0 | 0 |
| $\bar{x}y$       | 0 | 1 |
| $x\bar{y}$       | 1 | 0 |
| $xy$             | 1 | 1 |

# Minterms

- Function with three inputs?
- Minterms are similar...
- Just imagine counting in binary to find all the minterms...

| Minterm                 | X | Y | Z |
|-------------------------|---|---|---|
| $\bar{X}\bar{Y}\bar{Z}$ | 0 | 0 | 0 |
| $\bar{X}\bar{Y}Z$       | 0 | 0 | 1 |
| $\bar{X}Y\bar{Z}$       | 0 | 1 | 0 |
| $\bar{X}YZ$             | 0 | 1 | 1 |
| $X\bar{Y}\bar{Z}$       | 1 | 0 | 0 |
| $X\bar{Y}Z$             | 1 | 0 | 1 |
| $XY\bar{Z}$             | 1 | 1 | 0 |
| $XYZ$                   | 1 | 1 | 1 |

# Introduction to Karnaugh Maps

- A Kmap has a cell for each minterm
  - Cell for each line for the truth table of a function
- The truth table for the function  $F(x,y) = xy$  is shown along with its corresponding Kmap

$$F(X, Y) = XY$$

| X | Y | XY |
|---|---|----|
| 0 | 0 | 0  |
| 0 | 1 | 0  |
| 1 | 0 | 0  |
| 1 | 1 | 1  |

|   |   | Y |   |
|---|---|---|---|
|   |   | 0 | 1 |
| X | 0 | 0 | 0 |
|   | 1 | 0 | 1 |

# Introduction to Karnaugh Maps

- Truth table and Kmap for the function  $F(x,y) = x + y$
- This function is equivalent to the OR of all of the minterms that have a value of 1

$$F(X, Y) = X + Y$$

| X | Y | X+Y |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 1   |
| 1 | 0 | 1   |
| 1 | 1 | 1   |

$$F(x, y) = x + y = \bar{x}y + x\bar{y} + xy$$

|   |   | Y |   |
|---|---|---|---|
|   |   | 0 | 1 |
| X | 0 | 0 | 1 |
|   | 1 | 1 | 1 |

# Introduction to Karnaugh Maps

- Minterm function derived from Kmap was not in simplest terms
- Use Kmap to reduce expression to simplest terms
  - Find **adjacent 1's** in the Kmap that can be collected into groups that are **powers of two**

Two groups in this example:

|   | Y | 0 | 1 |
|---|---|---|---|
| X |   |   |   |
| 0 |   | 0 | 1 |
| 1 |   | 1 | 1 |

# Introduction to Karnaugh Maps

- Selected groups shown below
  - Groups are powers of two (# of elements)
  - Overlapping is OK!

| X \ Y | 0 | 1 |
|-------|---|---|
| 0     | 0 | 1 |
| 1     | 1 | 1 |



# Rules for Simplification

- Groupings can contain only 1's; no 0's
- Groups can be formed only at right angles
  - Diagonal groups are not allowed
- The number of 1's in a group must be a power of 2
  - A single 1 is OK then, but not three 1's!
- Groups must be made as large as possible
  - Otherwise simplification is incomplete
- Groups can overlap
- Groups can wrap around the sides of the Kmap

# Kmap – Three Variables

- Extend to three variables? Easy!
- **Warning!** Note that the values for the yz combination at the top of the matrix form a pattern that is **not a normal binary sequence**
  - **Each position can only differ by 1 variable**

|   |   | YZ                      |                   |             |                   |
|---|---|-------------------------|-------------------|-------------|-------------------|
|   |   | 00                      | 01                | 11          | 10                |
| X | 0 | $\bar{X}\bar{Y}\bar{Z}$ | $\bar{X}\bar{Y}Z$ | $\bar{X}YZ$ | $\bar{X}Y\bar{Z}$ |
|   | 1 | $X\bar{Y}\bar{Z}$       | $X\bar{Y}Z$       | $XYZ$       | $XY\bar{Z}$       |

# Kmap – Three Variables

- What do the values look like?
  - First row contains all minterms where x has a value of zero.
  - First column contains all minterms where y and z both have a value of zero

| x | YZ                      |                   |             |                   |
|---|-------------------------|-------------------|-------------|-------------------|
|   | 00                      | 01                | 11          | 10                |
| 0 | $\bar{x}\bar{y}\bar{z}$ | $\bar{x}\bar{y}z$ | $\bar{x}yz$ | $\bar{x}y\bar{z}$ |
| 1 | $x\bar{y}\bar{z}$       | $x\bar{y}z$       | $xyz$       | $xy\bar{z}$       |

# Kmap – Three Variables

➤ Example:

$$F(X, Y, Z) = \bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XYZ$$

➤ Kmap:

| X \ YZ | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 0  | 1  | 1  | 0  |
| 1      | 0  | 1  | 1  | 0  |

➤ What is the largest group of 1's that is a power of 2?

# Kmap – Three Variables

- Look at the grouping closely
  - Changes in the variables x and y have no influence upon the value of the function
  - Thus, the function

$$F(X, Y) = \bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XYZ$$

- reduces to  $F(x) = z$

You could verify this reduction with identities or a truth table

|   |   | YZ |    |    |    |
|---|---|----|----|----|----|
|   |   | 00 | 01 | 11 | 10 |
| X | 0 | 0  | 1  | 1  | 0  |
|   | 1 | 0  | 1  | 1  | 0  |

# Kmap – Three Variables

➤ Example:

$$F(X, Y, Z) = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}YZ + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z}$$

➤ Kmap:

| X \ YZ | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 1  | 1  | 1  | 1  |
| 1      | 1  | 0  | 0  | 1  |

➤ **What are the largest groups of 1's that are a power of 2?**

➤ **How many groups do you see?**

# Kmap – Three Variables

- To make the **largest groups possible**, wrap around the sides
- **How do we interpret results?**
  - Green row?
  - Pink square?

|   | YZ | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| X | 0  | 1  | 1  | 1  | 1  |
| 1 | 1  | 1  | 0  | 0  | 1  |

The Karnaugh map shows a green row highlighting the top row (X=0) and a pink square highlighting the four corners (X=0, YZ=00 and 10; X=1, YZ=00 and 10). A yellow background highlights the entire map area.

# Kmap – Three Variables

- Green group – only the value of x is significant
  - Thus,  $\bar{X}$
- Pink group – only the value of z is significant
- Our reduced function is:  $F(X, Y, Z) = \bar{X} + \bar{Z}$

Recall that we had six minterms in our original function!

|   | YZ | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| X | 0  | 1  | 1  | 1  | 1  |
| 1 | 1  | 1  | 0  | 0  | 1  |



# Kmap – Four Variables

- Model can be extended to accommodate a four-input function
  - 16 minterms produced

|    |    | YZ                             |                          |                    |                          |
|----|----|--------------------------------|--------------------------|--------------------|--------------------------|
|    |    | 00                             | 01                       | 11                 | 10                       |
| WX | 00 | $\bar{W}\bar{X}\bar{Y}\bar{Z}$ | $\bar{W}\bar{X}\bar{Y}Z$ | $\bar{W}\bar{X}YZ$ | $\bar{W}\bar{X}Y\bar{Z}$ |
|    | 01 | $\bar{W}X\bar{Y}\bar{Z}$       | $\bar{W}X\bar{Y}Z$       | $\bar{W}XYZ$       | $\bar{W}XY\bar{Z}$       |
|    | 11 | $WX\bar{Y}\bar{Z}$             | $WX\bar{Y}Z$             | $WXYZ$             | $WXY\bar{Z}$             |
|    | 10 | $W\bar{X}\bar{Y}\bar{Z}$       | $W\bar{X}\bar{Y}Z$       | $W\bar{X}YZ$       | $W\bar{X}Y\bar{Z}$       |

# Kmap – Four Variables

➤ Example:  $F(W, X, Y, Z) = \bar{W}\bar{X}\bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Y}Z + \bar{W}\bar{X}Y\bar{Z} + \bar{W}\bar{X}YZ + \bar{W}XY\bar{Z} + \bar{W}XYZ + W\bar{X}\bar{Y}\bar{Z} + W\bar{X}\bar{Y}Z + W\bar{X}Y\bar{Z} + W\bar{X}YZ$

➤ Kmap (showing non-zero terms)

➤ **What largest groups should we select?**

➤ Groups can overlap!

➤ Groups can wrap!

|    |    | YZ |    |    |    |
|----|----|----|----|----|----|
|    |    | 00 | 01 | 11 | 10 |
| WX | 00 | 1  | 1  |    | 1  |
|    | 01 |    |    |    | 1  |
|    | 11 |    |    |    |    |
|    | 10 | 1  | 1  |    | 1  |

# Kmap – Four Variables

## ➤ Three groups

1. Pink group that wraps top and bottom
2. Green group that spans the corners
3. Purple group entirely within the Kmap at the right

| WX \ YZ | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 1  |    | 1  |
| 01      |    |    |    | 1  |
| 11      |    |    |    |    |
| 10      | 1  | 1  |    | 1  |

The Kmap shows three groups: a pink group wrapping from the top row (WX=00) to the bottom row (WX=10) for YZ=00 and 01; a green group wrapping from the top-left corner (WX=00, YZ=00) to the bottom-right corner (WX=10, YZ=10); and a purple group in the right column (YZ=10) for WX=00 and 01.

$$F(W, X, Y, Z) = \bar{X}\bar{Y} + \bar{X}\bar{Z} + \bar{W}Y\bar{Z}$$

# Kmap – Four Variables

- Kmap simplification may not be unique
  - Possible to have different largest possible groups...
- The (different) functions that result from the groupings below are logically equivalent

|    |    | YZ |    |    |    |
|----|----|----|----|----|----|
|    |    | 00 | 01 | 11 | 10 |
| WX | 00 | 1  |    | 1  |    |
|    | 01 | 1  |    | 1  | 1  |
|    | 11 | 1  |    |    |    |
|    | 10 | 1  |    |    |    |

Groupings in the first Kmap: a vertical green group (WX=00, WX=01, WX=11, WX=10, YZ=00), a vertical blue group (WX=00, WX=01, WX=11, WX=10, YZ=11), and a horizontal pink group (WX=00, WX=01, YZ=10).

|    |    | YZ |    |    |    |
|----|----|----|----|----|----|
|    |    | 00 | 01 | 11 | 10 |
| WX | 00 |    |    | 1  |    |
|    | 01 |    |    | 1  | 1  |
|    | 11 |    |    |    |    |
|    | 10 |    |    |    |    |

Groupings in the second Kmap: a vertical blue group (WX=00, WX=01, WX=11, WX=10, YZ=00), a vertical green group (WX=00, WX=01, YZ=11), and a horizontal pink group (WX=00, WX=01, YZ=10).

# Don't Care Conditions



- Real circuits don't always need to have an output defined for every possible input
  - Example: Calculator displays have 7-segment LEDs. These LEDs can display  $2^7-1$  patterns, but only ten of them are useful
  
- If a circuit is designed so that a particular set of inputs can never happen, we call this set of inputs a don't care condition
  - Helpful for Kmap circuit simplification

# Don't Care Conditions

- Represent a don't care condition with an X
- Free to include or ignore the X's when choosing groups

| WX \ YZ | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | X  | 1  | 1  | X  |
| 01      |    | X  | 1  |    |
| 11      | X  |    | 1  |    |
| 10      |    |    | 1  |    |

# Don't Care Conditions

➤ Grouping option #1:

|    |    | YZ |    |    |    |
|----|----|----|----|----|----|
|    |    | 00 | 01 | 11 | 10 |
| WX | 00 | X  | 1  | 1  | X  |
|    | 01 |    | X  | 1  |    |
|    | 11 | X  |    | 1  |    |
|    | 10 |    |    | 1  |    |
|    |    |    |    | 1  |    |

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

# Don't Care Conditions

➤ Grouping option #2:

|    |    | YZ |    |    |    |
|----|----|----|----|----|----|
|    |    | 00 | 01 | 11 | 10 |
| WX | 00 | X  | 1  | 1  | X  |
|    | 01 |    | X  | 1  |    |
|    | 11 | X  |    | 1  |    |
|    | 10 |    |    | 1  |    |
|    |    |    |    | 1  |    |

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$



# Don't Care Conditions

➤ The truth table of

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

➤ differs from the truth table of

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$

➤ However, the values for which they differ are the inputs for which we have don't care conditions

➤ **Either is an acceptable solution**