



Computer Systems and Networks

ECPE 170 – Jeff Shafer – University of the Pacific

Exam 1 Review

Exam 1 Basics

➤ Topics

- Chapter 2
 - Data representations
- Chapter 3
 - Digital logic

➤ Rules

- No calculators
- Closed book / notes / friend / Internet / etc...

Review Materials

- Things to study
 - Homework assignments
 - **Solutions are posted in Sakai**
 - Quiz 1 and 2
 - **Solutions are posted in Sakai**
 - Lecture notes
- Question format will be similar to quizzes
 - Mix of problems and short answer questions
 - *Problems typically come from textbook...*
 - *Short answer questions typically come from lectures...*

Chapter 2 – Data Representation



Number Formats

➤ **Convert 26.78125_{10} to binary (max of 6 digits after binary point)**

➤ **Ans: 11010.11001**

Number Formats

➤ **Convert 110010011101_2 to hexadecimal**

➤ **Ans: $C9D_{16}$**

Number Formats

- **Express 23_{10} and -9_{10} in 8-bit binary using signed-magnitude, 1's complement, and 2's complement format**

- Ans for 23:
 - Signed-magnitude: 00010111_2
 - One's comp: 00010111_2
 - Two's comp: 00010111_2

- Ans for -9
 - Signed-magnitude: 10001001_2
 - One's comp: 11110110_2
 - Two's comp: 11110111_2

Number Formats

- **Convert 26.78125_{10} to IEEE 754 single-precision floating-point format**
(recall that $26.78125_{10} = 11010.11001$)
- Ans:
 - Sign bit: 0 (i.e. positive)
 - Exponent: 10000011 (i.e. $127+4=131$)
 - Significand: 1010110010...0 (for 23 bits)

Data Representation

- **What is ASCII? EBCDIC? Unicode?**
 - **What do they do the same? Different?**
 - **Why are there three standards?**

Chapter 3 – Digital Logic



Boolean Expressions

- **In the Boolean expression $F(x,y)=x+y$, does this mean “add the value to x to the value of y ?”**
 - No: the $+$ operator is OR!
- **Order of operations: what do I do first? Second?**

$$F(x, y, z) = \overline{xyz}$$

- Equivalent way to write it:

$$F(x, y, z) = (xyz)'$$

Boolean Expression

➔ **Simplify the following Boolean expression:**

$$F(x, y, z) = xy + \bar{x}z + yz$$

$$F(x, y, z) = xy + \bar{x}z + (x + \bar{x})yz$$

$$F(x, y, z) = xy + \bar{x}z + xyz + \bar{x}yz$$


$$F(x, y, z) = xy + xyz + \bar{x}z + \bar{x}yz$$

$$F(x, y, z) = xy(1 + z) + \bar{x}z(1 + y)$$

$$F(x, y, z) = xy + \bar{x}z$$


Digital Logic

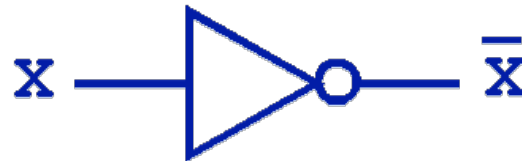- **What is this gate?**
- **What is its truth table?**




Digital Logic

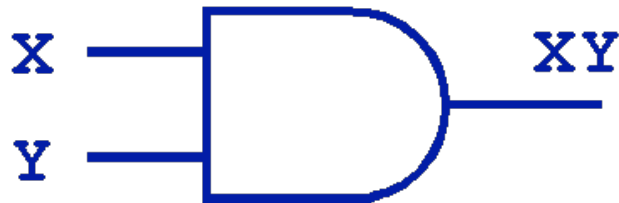- **What is this gate?**
- **What is its truth table?**




Digital Logic

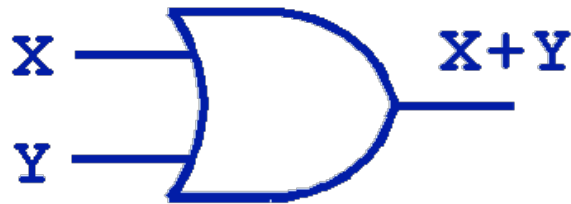- **What is this gate?**
- **What is its truth table?**




Digital Logic

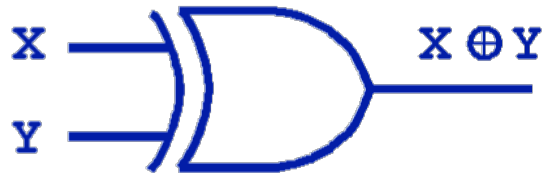- **What is this gate?**
- **What is its truth table?**




Digital Logic

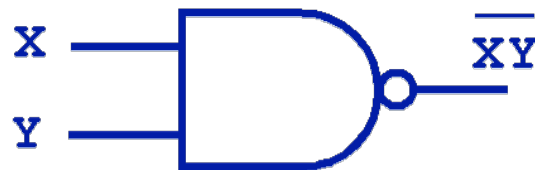- **What is this gate?**
- **What is its truth table?**




Digital Logic

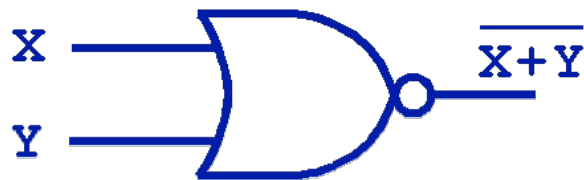- **What is this gate?**
- **What is its truth table?**



Digital Logic

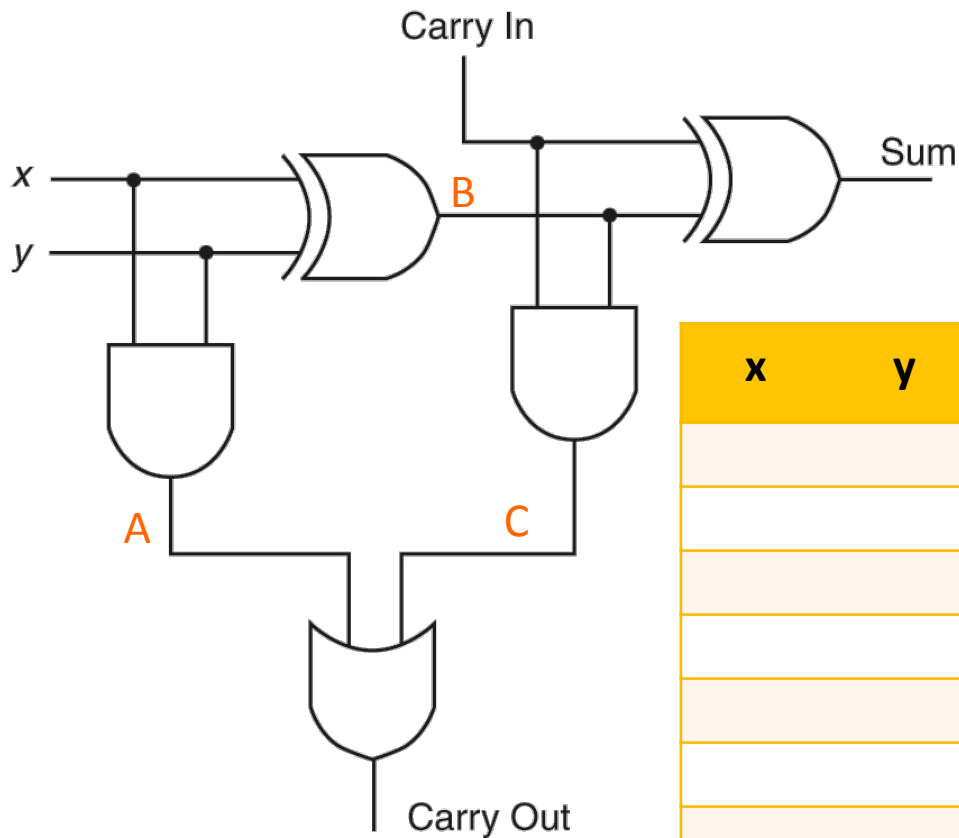

➔ Draw the truth table for this circuit

➔ What is this circuit?

x	y	Cin	A	B	C	Sum	Cout

Digital Logic – Sequential

- **Give the truth table for an SR, JK, and D flip flop**
 - **What does SR mean?**
 - **What does JK mean?**
 - **What does D mean?**

Karnaugh Maps

w	x	y	z	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

➔ **Construct a K-map from the truth table**

➔ **Simplify the resulting function**

$$F(w,x,y,z) = yz + xz + w'x'y'z' + wx'y$$